All problems refer to the following flowgraph ( $Y = x^* a0 + x@1 * b1$ )



## 1. Assume the multiplier now has a pipeline stage, and apply this to the schedule on the previous page.

	Sample A	Sample B	Sample C	Sample D	Sample E
Clk N	N1(← )				
Clk N+1	N2(*),N3(*)	N1(← )			
Clk N+2	• •	N2(*),N3(*)	N1(← )		
Clk N+3	N4(+)	↓ ↓	N2(*),N3(*)	N1(← )	
Clk N+4		N4(+)	<b>★ ★</b>	N2(*),N3(*)	N1(← )
Clk N+5			N4(+)	• •	N2(*),N3(*)
Clk N+6				N4(+)	$\downarrow$ $\downarrow$ $\downarrow$
Clk N+7					N4(+)

What happens to the latency?

Does the datapath need to change other than replacing the multiplier with a pipelined multiplier? Why or Why not?

No, it does not need to change since the pipeline stages add the same latency to every path.

## 2. Assume the delay of the multiplier is 20 ns, the adder delay is 7 ns, Tsu = 1 ns, Thd = 1 ns, TCq = 2ns

A1. What is the minimum clock period of the original datapath? Tmult + Tcq + Tsu = 20 + 2 + 1 = 23 ns

A2. How long does it take to compute the first 10 sample values? Include pipeline startup.

3 clocks for 1 sample, then 9 clocks after that. 3 \* 23 + 9\*23 = 276 ns

B1. What is the minimum clock period of the new datapath with the pipelined multiplier?

Tmult/2 + Tcq + Tsu = 10 + 2 + 1 = 13 ns

How long does it take to compute 10 sample values?

4 clocks for 1 sample, 9 clocks after that : 4 \* 13 + 9 \* 13 = 169 ns.

The schedule for flowgraph with the Y @1 input value is shown below.

	Sample J	Sample J+1	Figure 2
Clk 1	NI		N1
Clk 2	N3, N2 (depends on N4		
	Sample J-1)		$\begin{bmatrix} A \\ A \end{bmatrix} = \begin{bmatrix} A $
Clk 3	N4	N1,	
Clk 4		→N3, N2	
		(depends on N4 sample J)	N3 N4
Clk 5		N4	(+)►
Clk 6			] Y
			- ↓ Y



## 3. Assume the multiplier now has a pipeline stage, and create a new schedule. What happens to initiation rate, latency?

	Sample A	Sample B	Sample C	Sample D	Sample E
Clk N	N1				
Clk N+1	N3, N2				
Clk N+2	↓ ↓				
Clk N+3	N4	N1			
Clk N+4		N3,N2			
Clk N+5		•			
Clk N+6		N4			
Clk N+7					



## 4. Assume the delay of the multiplier is 20 ns, the adder delay is 7 ns, Tsu = 1 ns, Thd = 1 ns, TCq = 2ns

A1. What is the minimum clock period of the original datapath (without pipelining)?

Tmult + Tcq + Tsu = 20 + 2 + 1 = 23 ns

A2. How long does it take to compute the first 10 sample values (without a pipelined multiplier)? Include datapath startup.

3 clocks for first sample, then 9\*2 clocks after that. 3\*23 + 9\*2\*23 = 483 ns

B1. What is the minimum clock period of the new datapath with the pipelined multiplier?

Tmult/2 + Tcq + Tsu = 10 + 2 + 1 = 13 ns

How long does it take to compute 10 sample values?

4 clocks for first sample, then 9\*3 clocks after that. 4\*13 + 9\*3\*13 = 403 ns