

Outline

Combinational Circuit Design: Practice

1. Derivation of efficient HDL description
2. Operator sharing
3. Functionality sharing
4. Layout-related circuits
5. General circuits

1. Derivation of efficient HDL description

- Think “H”, not “L”, of HDL
- Right way:
 - Research to find an efficient design (“domain knowledge”)
 - Develop VHDL code that accurately describes the design
- Wrong way:
 - Write a C program and convert it to HDL

Sharing

- Circuit complexity of VHDL operators varies
- Arith operators
 - Large implementation
 - Limited optimization by synthesis software
- “Optimization” can be achieved by “sharing” in RT level coding
 - Operator sharing
 - Functionality sharing

An example 0.55 um standard-cell CMOS implementation

width	VHDL operator									
	nand	xor	> _a	> _d	=	+1 _a	+1 _d	+ _a	+ _d	mux
area (gate count)										
8	8	22	25	68	26	27	33	51	118	21
16	16	44	52	102	51	55	73	101	265	42
32	32	85	105	211	102	113	153	203	437	85
64	64	171	212	398	204	227	313	405	755	171
delay (ns)										
8	0.1	0.4	4.0	1.9	1.0	2.4	1.5	4.2	3.2	0.3
16	0.1	0.4	8.6	3.7	1.7	5.5	3.3	8.2	5.5	0.3
32	0.1	0.4	17.6	6.7	1.8	11.6	7.5	16.2	11.1	0.3
64	0.1	0.4	35.7	14.3	2.2	24.0	15.7	32.2	22.9	0.3

2. Operator sharing

- “value expressions” in priority network and multiplexing network are mutually exclusively:
- Only one result is routed to output
- Conditional sig assignment (if statement)


```
sig_name <= value_expr_1 when boolean_expr_1 else
          value_expr_2 when boolean_expr_2 else
          value_expr_3 when boolean_expr_3 else
          ...
          value_expr_n;
```

Example 1

- Selected sig assignment (case statement)


```
with select_expression select
    sig_name <= value_expr_1 when choice_1,
    value_expr_2 when choice_2,
    value_expr_3 when choice_3,
    ...
    value_expr_n when choice_n;
```

- Original code:

```
r <= a+b when boolean_exp else
    a+c;
```

- Revised code:
 
```
src0 <= b when boolean_exp else
    c;
r <= a + src0;
```



Area: 2 adders, 1 mux
Delay:

$$\max(T_{adder}, T_{boolean}) + T_{mux}$$

Area: 1 adder, 1 mux
Delay:

$$T_{boolean} + T_{mux} + T_{adder}$$


Example 2

- Original code:

```
process(a,b,c,d,...)
begin
    if boolean_exp_1 then
        r <= a+b;
    elsif boolean_exp_2 then
        r <= a+c;
    else
        r <= d+1;
    end if
end process;
```

- Revised code:
 
```
process(a,b,c,d,...)
begin
    if boolean_exp_1 then
        src0 <= a;
        src1 <= b;
    elsif boolean_exp_2 then
        src0 <= a;
        src1 <= c;
    else
        src0 <= d;
        src1 <= "00000001";
    end if;
end process;
r <= src0 + src1;
```



Area:
2 adders, 1 inc, 2 mux

Area:
1 adder, 4 mux

Example 3

- Original code:


```
with sel select
    r <= a+b when "00",
    a+c when "01",
    d+1 when others;
```
- Revised code:

```
with sel_exp select
    src0 <= a when "00"|"01",
    d when others;
with sel_exp select
    src1 <= b when "00",
    c when "01",
    "00000001" when others;
r <= src0 + src1;
```

RTL Hardware Design
by P. Chu

Chapter 7

13

 

(a) Original diagram

(b) Diagram with sharing

Area:
2 adders, 1 inc, 1 mux

Area:
1 adder, 2 mux

RTL Hardware Design
by P. Chu

Chapter 7

14

Example 4


- Original code:

```
process(a,b,c,d,...)
begin
    if boolean_exp then
        x <= a + b;
        y <= (others=>'0');
    else
        x <= (others=>'1');
        y <= c + d;
    end if;
end process;
```

RTL Hardware Design
by P. Chu

Chapter 7

15

 

(a) Original diagram

Area:
2 adders, 2 mux

RTL Hardware Design
by P. Chu

Chapter 7

16


- Revised code:

```
begin
    if boolean_exp then
        src0 <= a;
        src1 <= b;
        x <= sum;
        y <= (others=>'0');
    else
        src0 <= c;
        src1 <= d;
        x <= (others=>'1');
        y <= sum;
    end if;
end process;
sum <= src0 + src1;
```

RTL Hardware Design
by P. Chu

Chapter 7

17

 

- Area: 1 adder, 4 mux
- Is the sharing worthwhile?
 - 1 adder vs 2 mux
 - It depends . . .

RTL Hardware Design
by P. Chu

Chapter 7

18

Summary

- Sharing is done by additional routing circuit
- Merit of sharing depends on the complexity of the operator and the routing circuit
- Ideally, synthesis software should do this

RTL Hardware Design
by P. Chu

Chapter 7

19

3. Functionality sharing

- A large circuit involves lots of functions
- Several functions may be related and have common characteristics
- Several functions can share the same circuit.
- Done in an “ad hoc” basis, based on the understanding and insight of the designer (i.e., “domain knowledge”)
- Difficult for software since it does not know the “meaning” of functions

RTL Hardware Design
by P. Chu

Chapter 7

20

e.g., add-sub circuit

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity addsub is
port (
    a,b: in std_logic_vector(7 downto 0);
    ctrl: in std_logic;
    r: out std_logic_vector(7 downto 0)
);
end addsub;

architecture direct_arch of addsub is
    signal src0, src1, sum: signed(7 downto 0);
begin
    src0 <= signed(a);
    src1 <= signed(b);
    sum <= src0 + src1 when ctrl='0' else
        src0 - src1;
    r <= std_logic_vector(sum);
end direct_arch;
```

21

ctrl	operation
0	a + b
1	a - b

- Manual injection of carry-in:
- Append an additional bit in right (LSB):

```
x7x6x5x4x3x2x1x01 and y7y6y5y4y3y2y1y0cin
architecture manual_carry_arch of addsub is
    signal src0, src1, sum: signed(8 downto 0);
    signal b_tmp: std_logic_vector(7 downto 0);
    signal cin: std_logic; — carry-in bit
begin
    src0 <= signed(a & '1');
    b_tmp <= b when ctrl='0' else
        not b;
    cin <= '0' when ctrl='0' else
        '1';
    src1 <= signed(b_tmp & cin);
    sum <= src0 + src1;
    r <= std_logic_vector(sum(8 downto 1));
end manual_carry_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

23


- Observation: $a - b$ can be done by $a + b' + 1$

```
architecture shared_arch of addsub is
    signal src0, src1, sum: signed(7 downto 0);
    signal cin: signed(0 downto 0); — carry-in bit
begin
    src0 <= signed(a);
    src1 <= signed(b) when ctrl='0' else
        signed(not b);
    cin <= "0" when ctrl='0' else
        "1";
    sum <= src0 + src1 + cin;
    r <= std_logic_vector(sum);
end shared_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

22

 

RTL Hardware Design
by P. Chu

Chapter 7

24

e.g., sign-unsigned comparator

```


library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity comp2mode is
  port(
    a,b: in std_logic_vector(7 downto 0);
    mode: in std_logic;
    agtb: out std_logic
  );
end comp2mode;

architecture direct_arch of comp2mode is
  signal agtb_signed, agtb_unsigned: std_logic;
begin
  agtb_signed <= '1' when signed(a) > signed(b) else
    '0';
  agtb_unsigned <= '1' when unsigned(a) > unsigned(b) else
    '0';
  agtb <= agtb_unsigned when (mode='0') else
    agtb_signed;
end direct_arch;

```

Binary wheel

 

26

- Observation:

- Unsigned: normal comparator
- Signed:
 - Different sign bit: positive number is larger
 - Same sign: compare remaining 3 LSBs
This works for negative number, too!
E.g., 1111 (-1), 1100 (-4), 1001 (-7)
111 > 100 > 001

- The comparison of 3 LSBs can be shared

RTL Hardware Design
by P. Chu

Chapter 7

27

```

architecture shared_arch of comp2mode is
  signal a1_b0, agtb_mag: std_logic;
begin
  a1_b0 <= '1' when a(7)='1' and b(7)='0' else
    '0';
  agtb_mag <= '1' when a(6 downto 0) > b(6 downto 0) else
    '0';
  agtb <= agtb_mag when (a(7)=b(7)) else
    a1_b0 when mode='0' else
    not a1_b0;
end shared_arch;

```

RTL Hardware Design
by P. Chu

Chapter 7

28

e.g., Full comparator

```

library ieee;
use ieee.std_logic_1164.all;
entity comp3 is
  port(
    a,b: in std_logic_vector(15 downto 0);
    agtb, altb, aeqb: out std_logic
  );
end comp3;

architecture direct_arch of comp3 is
begin
  agtb <= '1' when a > b else
    '0';
  altb <= '1' when a < b else
    '0';
  aeqb <= '1' when a = b else
    '0';
end direct_arch;

```

RTL Hardware Design
by P. Chu

Chapter 7

29

```

architecture share1_arch of comp3 is
  signal gt, lt: std_logic;
begin
  gt <= '1' when a > b else
    '0';
  lt <= '1' when a < b else
    '0';
  agtb <= gt;
  altb <= lt;
  aeqb <= not (gt or lt);
end share1_arch;

```

RTL Hardware Design
by P. Chu

Chapter 7

30

```

architecture share2_arch of comp3 is
  signal eq, lt: std_logic;
begin
  eq <= '1' when a = b else
    '0';
  lt <= '1' when a < b else
    '0';
  aeqb <= eq;
  altb <= lt;
  agtb <= not (eq or lt);
end share2_arch;



```

- Read 7.3.3 and 7.3.5

  4. Layout-related circuits

- After synthesis, placement and routing will derive the actual physical layout of a digital circuit on a silicon chip.
- VHDL cannot specify the exact layout
- VHDL can outline the general “shape”

- Silicon chip is a “square”
- “Two-dimensional” shape (tree or rectangular) is better than one-dimensional shape (cascading-chain)
- Conditional signal assignment/if statement form a single “horizontal” cascading chain
- Selected signal assignment/case statement form a large “vertical” mux
- Neither is ideal



e.g., Reduced-xor circuit

```


$$a_7 \oplus a_6 \oplus a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0$$


library ieee;
use ieee.std_logic_1164.all;

entity reduced_xor is
  port (
    a: in std_logic_vector(7 downto 0);
    y: out std_logic
  );
end reduced_xor;

architecture cascade1_arch of reduced_xor is
begin
  y <= a(0) xor a(1) xor a(2) xor a(3) xor
      a(4) xor a(5) xor a(6) xor a(7);
end cascade1_arch;

```

RTL Hardware Design
by P. Chu

Chapter 7

37

```

architecture cascade2_arch of reduced_xor is
  signal p: std_logic_vector(7 downto 0);
begin
  p(0) <= a(0);                                p(0) <= '0' xor a(0);
  p(1) <= p(0) xor a(1);                      p(1) <= p(0) xor a(1);
  p(2) <= p(1) xor a(2);                      p(2) <= p(1) xor a(2);
  p(3) <= p(2) xor a(3);                      p(3) <= p(2) xor a(3);
  p(4) <= p(3) xor a(4);                      p(4) <= p(3) xor a(4);
  p(5) <= p(4) xor a(5);                      p(5) <= p(4) xor a(5);
  p(6) <= p(5) xor a(6);                      p(6) <= p(5) xor a(6);
  p(7) <= p(6) xor a(7);                      p(7) <= p(6) xor a(7);
  y <= p(7);
end cascade2_arch;


architecture cascade_compact_arch of reduced_xor is
  constant WIDTH: integer := 8;
  signal p: std_logic_vector(WIDTH-1 downto 0);
begin
  p <= (p(WIDTH-2 downto 0) & '0') xor a;
  y <= p(WIDTH-1);
end cascade_compact_arch;

```

RTL Hardware Design
by P. Chu

Chapter 7

38

 

RTL Hardware Design
by P. Chu


Chapter 7

39

```

architecture tree_arch of reduced_xor is
begin
  y <= ((a(7) xor a(6)) xor (a(5) xor a(4))) xor
        ((a(3) xor a(2)) xor (a(1) xor a(0)));
end tree_arch;

```

 

RTL Hardware Design
by P. Chu

Chapter 7

40

- Comparison of n-input reduced xor
 - Cascading chain :
 - Area: $(n-1)$ xor gates
 - Delay: $(n-1)$
 - Coding: easy to modify (scale)
 - Tree:
 - Area: $(n-1)$ xor gates
 - Delay: $\log_2 n$
 - Coding: not so easy to modify
 - Software should able to do the conversion automatically

e.g., Reduced-xor-vector circuit

$$\begin{aligned}
 y_0 &= a_0 \\
 y_1 &= a_1 \oplus a_0 \\
 y_2 &= a_2 \oplus a_1 \oplus a_0 \\
 y_3 &= a_3 \oplus a_2 \oplus a_1 \oplus a_0 \\
 y_4 &= a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0 \\
 y_5 &= a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0 \\
 y_6 &= a_6 \oplus a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0 \\
 y_7 &= a_7 \oplus a_6 \oplus a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0
 \end{aligned}$$

RTL Hardware Design
by P. Chu

Chapter 7

41

RTL Hardware Design
by P. Chu

Chapter 7

42

- Direct implementation

```
entity reduced_xor_vector is
  port(
    a: in std_logic_vector(7 downto 0);
    y: out std_logic_vector(7 downto 0)
  );
end reduced_xor_vector;

architecture direct_arch of reduced_xor_vector is
  signal p: std_logic_vector(7 downto 0);
begin
  y(0) <= a(0);
  y(1) <= a(1) xor a(0);
  y(2) <= a(2) xor a(1) xor a(0);
  y(3) <= a(3) xor a(2) xor a(1) xor a(0);
  y(4) <= a(4) xor a(3) xor a(2) xor a(1) xor a(0);
  y(5) <= a(5) xor a(4) xor a(3) xor a(2) xor a(1) xor a(0);
  y(6) <= a(6) xor a(5) xor a(4) xor a(3) xor a(2) xor a(1) xor a(0);
  y(7) <= a(7) xor a(6) xor a(5) xor a(4) xor a(3) xor a(2) xor a(1) xor a(0);
end direct_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

43

- Functionality Sharing

```
architecture shared1_arch of reduced_xor_vector is
  signal p: std_logic_vector(7 downto 0);
begin
  p(0) <= a(0);
  p(1) <= p(0) xor a(1);
  p(2) <= p(1) xor a(2);
  p(3) <= p(2) xor a(3);
  p(4) <= p(3) xor a(4);
  p(5) <= p(4) xor a(5);
  p(6) <= p(5) xor a(6);
  p(7) <= p(6) xor a(7);
  y <= p;
end shared1_arch;

architecture shared_compact_arch of reduced_xor_vector is
  constant WIDTH: integer := 8;
  signal p: std_logic_vector(WIDTH-1 downto 0);
begin
  p <= (p(WIDTH-2 downto 0) & '0') xor a;
  y <= p;
end shared_compact_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

44

- Direct tree implementation


```
architecture direct_tree_arch of reduced_xor_vector is
  signal p: std_logic_vector(7 downto 0);
begin
  y(0) <= a(0);
  y(1) <= a(1) xor a(0);
  y(2) <= a(2) xor a(1) xor a(0);
  y(3) <= (a(3) xor a(2)) xor (a(1) xor a(0));
  y(4) <= (a(4) xor a(3)) xor (a(2) xor a(1)) xor a(0);
  y(5) <= (a(5) xor a(4)) xor (a(3) xor a(2)) xor (a(1) xor a(0));
  y(6) <= ((a(6) xor a(5)) xor (a(4) xor a(3))) xor ((a(2) xor a(1)) xor a(0));
  y(7) <= (((a(7) xor a(6)) xor (a(5) xor a(4))) xor ((a(3) xor a(2)) xor (a(1) xor a(0))));
end direct_tree_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

45

- “Parallel-prefix” implementation

 

RTL Hardware Design
by P. Chu

Chapter 7

46

```
architecture optimal_tree_arch of reduced_xor_vector is
  signal p01, p23, p45, p67, p012,
  p0123, p456, p4567: std_logic;
begin
  p01 <= a(0) xor a(1);
  p23 <= a(2) xor a(3);
  p45 <= a(4) xor a(5);
  p67 <= a(6) xor a(7);
  p012 <= p01 xor a(2);
  p0123 <= p01 xor p23;
  p456 <= p45 xor a(6);
  p4567 <= p45 xor p67;
  y(0) <= a(0);
  y(1) <= p01;
  y(2) <= p012;
  y(3) <= p0123;
  y(4) <= p0123 xor a(4);
  y(5) <= p0123 xor p45;
  y(6) <= p0123 xor p456;
  y(7) <= p0123 xor p4567;
end optimal_tree_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

47

- Comparison of n-input reduced-xor-vector

- Cascading chain
 - Area: $(n-1)$ xor gates
 - Delay: $(n-1)$
 - Coding: easy to modify (scale)
- Multiple trees
 - Area: $O(n^2)$ xor gates
 - Delay: $\log_2 n$
 - Coding: not so easy to modify
- Parallel-prefix
 - Area: $O(n \log_2 n)$ xor gates
 - Delay: $\log_2 n$
 - Coding: difficult to modify
- Software is not able to convert cascading chain to parallel-prefix

RTL Hardware Design
by P. Chu

Chapter 7

48

e.g., Shifter (rotating right)

- Direct implementation


```
entity rotate_right is
port(
    a: in std_logic_vector(7 downto 0);
    amt: in std_logic_vector(2 downto 0);
    y: out std_logic_vector(7 downto 0)
);
end rotate_right;

architecture direct_arch of rotate_right is
begin
    with amt select
        y<= a when "000",
        a(0) & a(7 downto 1) when "001",
        a(1 downto 0) & a(7 downto 2) when "010",
        a(2 downto 0) & a(7 downto 3) when "011",
        a(3 downto 0) & a(7 downto 4) when "100",
        a(4 downto 0) & a(7 downto 5) when "101",
        a(5 downto 0) & a(7 downto 6) when "110",
        a(6 downto 0) & a(7) when others; -- lll
    end direct_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

49

 


RTL Hardware Design
by P. Chu

Chapter 7

50

- Better implementation

 

RTL Hardware Design
by P. Chu

Chapter 7

51

```
architecture multi_level_arch of rotate_right is
    signal le0_out, le1_out, le2_out:
        std_logic_vector(7 downto 0);
begin
    --- level 0, shift 0 or 1 bit
    le0_out <= a(0) & a(7 downto 1) when amt(0)='1' else
        a;
    --- level 1, shift 0 or 2 bits
    le1_out <=
        le0_out(1 downto 0) & le0_out(7 downto 2)
            when amt(1)='1' else
        le0_out;
    --- level 2, shift 0 or 4 bits
    le2_out <=
        le1_out(3 downto 0) & le1_out(7 downto 4)
            when amt(2)='1' else
        le1_out;
    y <= le2_out;
end multi_level_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

52

- Comparison for n-bit shifter

- Direct implementation

- n n-to-1 mux
- vertical strip with O(n²) input wiring
- Code not so easy to modify

- Staged implementation

- n*log₂n 2-to-1 mux
- Rectangular shaped
- Code easier to modify

5. General examples

- Gray code counter
- Signed addition with status
- Simple combinational multiplier

RTL Hardware Design
by P. Chu

Chapter 7

53

RTL Hardware Design
by P. Chu

Chapter 7

54

e.g., Gray code counter

binary code	gray code	gray code	incremented gray code
$b_3 b_2 b_1 b_0$	$g_3 g_2 g_1 g_0$		
0000	0000	0000	0001
0001	0001	0001	0011
0010	0011	0011	0010
0011	0010	0010	0110
0100	0110	0110	0111
0101	0111	0111	0101
0110	0101	0101	0100
0111	0100	0100	1100
1000	1100	1100	1101
1001	1101	1101	1111
1010	1111	1111	1110
1011	1110	1110	1010
1100	1010	1010	1011
1101	1011	1011	1001
1110	1001	1001	1000
1111	1000	1000	

RTL Hardware Design
by P. Chu

Chapter 7

55

- Direct implementation

```
entity g_inc is
  port(
    g: in std_logic_vector(3 downto 0);
    g1: out std_logic_vector(3 downto 0)
  );
end g_inc;

architecture table_arch of g_inc is
begin
  with g select
    g1 <= "0001" when "0000";
    "0011" when "0001";
    "0010" when "0011";
    "0110" when "0010";
    "0111" when "0110";
    "0101" when "0111";
    "0100" when "0101";
    "1100" when "0100";
    "1101" when "1100";
    "1110" when "1101";
    "1010" when "1110";
    "1011" when "1010";
    "1001" when "1011";
    "1000" when "1001";
    "0000" when others; -- "1000"
  end table_arch;
```

RTL Hardware Design
by P. Chu

56

- Observation

- Require 2^n rows
- No simple algorithm for gray code increment
- One possible method
 - Gray to binary
 - Increment the binary number
 - Binary to gray

RTL Hardware Design
by P. Chu

Chapter 7

57

- binary to gray

binary code	gray code
$b_3 b_2 b_1 b_0$	$g_3 g_2 g_1 g_0$
0000	0000
0001	0001
0010	0011
0011	0010
0100	0110
0101	0111
0110	0101
0111	0100
1000	1100
1001	1101
1010	1111
1011	1110
1100	1010
1101	1011
1110	1001
1111	1000

$$g_i = b_i \oplus b_{i+1}$$

$$g_3 = b_3 \oplus 0 = b_3$$

$$g_2 = b_2 \oplus b_3$$

$$g_1 = b_1 \oplus b_2$$

$$g_0 = b_0 \oplus b_1$$

- gray to binary

$$b_i = g_i \oplus b_{i+1}$$

$$b_3 = g_3 \oplus 0 = g_3$$

$$b_2 = g_2 \oplus b_3 = g_2 \oplus g_3$$

$$b_1 = g_1 \oplus b_2 = g_1 \oplus g_2 \oplus g_3$$

$$b_0 = g_0 \oplus b_1 = g_0 \oplus g_1 \oplus g_2 \oplus g_3$$

RTL Hardware Design
by P. Chu

Chapter 7

58

```
architecture compact_arch of g_inc is
  constant WIDTH: integer := 4;
  signal b, b1: std_logic_vector(WIDTH-1 downto 0);
begin
  — gray to binary
  b <= g xor ('0' & b(WIDTH-1 downto 1));
  — binary increment
  b1 <= std_logic_vector((unsigned(b)) + 1);
  — binary to gray
  g1<= b1 xor ('0' & b1(WIDTH-1 downto 1));
end compact_arch;
```

RTL Hardware Design
by P. Chu

Chapter 7

59

e.g., signed addition with status

- Adder with

- Carry-in: need an extra bit (LSB)
 - Carry-out: need an extra bit (MSB)
 - Overflow:
 - two operands has the same sign but the sum has a different sign
 - Zero
 - Sign (of the addition result)
- $$\text{overflow} = (s_a \cdot s_b \cdot s'_s) + (s'_a \cdot s'_b \cdot s_s)$$

RTL Hardware Design
by P. Chu

Chapter 7

60

e.g., simple combinational multiplier

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity adder_status is
  port (
    a,b: in std_logic_vector(7 downto 0);
    cin: in std_logic;
    sum: out std_logic_vector(7 downto 0);
    cout, zero, overflow, sign: out std_logic
  );
end adder_status;

architecture arch of adder_status is
  signal a_ext, b_ext, sum_ext: signed(9 downto 0);
  signal ovf: std_logic;
  alias sign_a: std_logic is a_ext(8);
  alias sign_b: std_logic is b_ext(8);
  alias sign_s: std_logic is sum_ext(8);
begin
  a_ext <= signed('0' & a & '1');
  b_ext <= signed('0' & b & cin);
  sum_ext <= a_ext + b_ext;
  ovf <- (sign_a and sign_b and (not sign_s)) or
          ((not sign_a) and (not sign_b) and sign_s);
  cout <= sum_ext(9);
  zero <= '1' when (sum_ext(8 downto 1)=0 and ovf='0') else
          '0';
  overflow <= ovf;
  sum <- std_logic_vector(sum_ext(8 downto 1));
end arch;

```

RTL Hardware Design
by P. Chu

Chapter 7

61

	\times	a_3	a_2	a_1	a_0	multiplicand
		b_3	b_2	b_1	b_0	multiplier
		a_3b_0	a_2b_0	a_1b_0	a_0b_0	
			a_3b_1	a_2b_1	a_1b_1	a_0b_1
			a_3b_2	a_2b_2	a_1b_2	a_0b_2
	$+$	a_3b_3	a_2b_3	a_1b_3	a_0b_3	
		y_7	y_6	y_5	y_4	y_3
				y_2	y_1	y_0
						product

RTL Hardware Design
by P. Chu

Chapter 7

62

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity mult8 is
  port(
    a, b: in std_logic_vector(7 downto 0);
    y: out std_logic_vector(15 downto 0)
  );
end mult8;
architecture comb1_arch of mult8 is
  constant WIDTH: integer:=8;
  signal au, bv0, bv1, bv2, bv3, bv4, bv5, bv6, bv7:
    unsigned(WIDTH-1 downto 0);
  signal p0,p1,p2,p3,p4,p5,p6,p7,prod:
    unsigned(2*WIDTH-1 downto 0);

```

RTL Hardware Design
by P. Chu

Chapter 7

63

```

begin
  au <= unsigned(a);
  bv0 <= (others=>b(0));
  bv1 <= (others=>b(1));
  bv2 <= (others=>b(2));
  bv3 <= (others=>b(3));
  bv4 <= (others=>b(4));
  bv5 <= (others=>b(5));
  bv6 <= (others=>b(6));
  bv7 <= (others=>b(7));
  p0 <="00000000" & (bv0 and au);
  p1 <="0000000" & (bv1 and au) & "0";
  p2 <="000000" & (bv2 and au) & "00";
  p3 <="00000" & (bv3 and au) & "000";
  p4 <="0000" & (bv4 and au) & "0000";
  p5 <="000" & (bv5 and au) & "00000";
  p6 <="00" & (bv6 and au) & "000000";
  p7 <="0" & (bv7 and au) & "0000000";
  prod <= ((p0+p1)+(p2+p3))+((p4+p5)+(p6+p7));
  y <= std_logic_vector(prod);
end comb1_arch;

```

RTL Hardware Design
by P. Chu

Chapter 7

64