

Register Transfer Methodology II


Outline

1. Design example: One-shot pulse generator
2. Design Example: GCD
3. Design Example: UART
4. Design Example: SRAM Interface Controller
5. Square root approximation circuit


1. One-shot pulse generator

- Sequential circuit divided into
 - Regular sequential circuit: w/ regular next-state logic
 - FSM: w/ random next-state logic
 - FSMD: w/ both
- Division for code development; no formal definition;
- Some design can be coded in different types
- FSMD is most flexible
- One-shot pulse generator as an example


- Basic block diagram

 


- Refined block diagram of FSMD

 

 - Regular sequential circuit. E.g., mod-10 counter



- FSM. E.g., edge-detection circuit

 

7


- FSMD.
E.g., multiplier



RTL Hardware Design
by P. Chu

- One-shot pulse generator
 - I/O: Input: go, stop; Output: pulse
 - go is the trigger signal, usually asserted for only one clock cycle
 - During normal operation, assertion of go activates pulse for 5 clock cycles
 - If go is asserted again during this interval, it will be ignored
 - If stop is asserted during this interval, pulse will be cut short and return to 0

- FSM implementation

 

RTL Hardware Design
by P. Chu

Chapter 12

9

RTL Hardware Design
by P. Chu

Chapter 12

10

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity pulse_5clk is
    port(
        clk, reset: in std_logic;
        go, stop: in std_logic;
        pulse: out std_logic
    );
end pulse_5clk;

architecture fsm_arch of pulse_5clk is
    type fsm_state_type is
        (idle, delay1, delay2, delay3, delay4, delay5);
    signal state_reg, state_next: fsm_state_type;
begin
    -- state register
    process(clk, reset)
    begin
        if (reset = '1') then
            state_reg <= idle;
        elsif (clk'event and clk = '1') then
            state_reg <= state_next;
        end if;
    end process;

```

RTL Hardware Design
by P. Chu

Chapter 12

11

```

-- next-state logic & output logic
process(state_reg, go, stop)
begin
    pulse <= '0';
    case state_reg is
        when idle =>
            if go = '1' then
                state_next <= delay1;
            else
                state_next <= idle;
            end if;
        when delay1 =>
            if stop = '1' then
                state_next <= idle;
            else
                state_next <= delay2;
            end if;
        when delay2 =>
            if stop = '1' then
                state_next <= idle;
            else
                state_next <= delay3;
            end if;
        when delay3 =>
            if stop = '1' then
                state_next <= idle;
            else
                state_next <= delay4;
            end if;
        when delay4 =>
            if stop = '1' then
                state_next <= idle;
            else
                state_next <= delay5;
            end if;
        when delay5 =>
            state_next <= idle;
        end case;
end process;

```

RTL Hardware Design
by P. Chu

Chapter 12

12

```

        state_next <= delay3;
    end if;
    pulse <= '1';
    when delay3 =>
        if stop='1' then
            state_next <= idle;
        else
            state_next <= delay4;
        end if;
    pulse <= '1';
    when delay4 =>
        if stop='1' then
            state_next <= idle;
        else
            state_next <= delay5;
        end if;
    pulse <= '1';
    when delay5 =>
        state_next <= idle;
        pulse <= '1';
    end case;
end process;
end fsm_arch;

```

RTL Hardware Design
by P. Chu

Chapter 12

13

- Regular sequential circuit implementation
 - Based on a mod-5 counter
 - Use a flag FF to indicate whether counter should be active
 - Code difficult to comprehend

```

architecture regular_seq_arch of pulse_5clk is
    constant P_WIDTH: natural:= 5;
    signal c_reg, c_next: unsigned(3 downto 0);
    signal flag_reg, flag_next: std_logic;
begin
    -- register
    process(clk,reset)
    begin
        if (reset='1') then
            c_reg <= (others=>'0');
            flag_reg <= '0';
        elsif (clk'event and clk='1') then
            c_reg <= c_next;
            flag_reg <= flag_next;
        end if;
    end process;
end regular_seq_arch;

```

RTL Hardware Design
by P. Chu

Chapter 12

14

```

-- next-state logic
process(c_reg,flag_reg,go,stop)
begin
    c_next <= c_reg;
    flag_next <= flag_reg;
    if (flag_reg='0') and (go='1') then
        flag_next <= '1';
        c_next <= (others=>'0');
    elsif (flag_reg='1') and
        ((c_reg=P_WIDTH-1) or (stop='1')) then
        flag_next <= '0';
    elsif (flag_reg='1') then
        c_next <= c_reg + 1;
    end if;
end process;
-- output logic
pulse <= '1' when flag_reg='1' else '0';
end regular_seq_arch;


```

RTL Hardware Design
by P. Chu

Chapter 12

15

- FSMD Implementation

 

RTL Hardware Design
by P. Chu

Chapter 12

16

```

architecture fsmd_arch of pulse_5clk is
    constant P_WIDTH: natural:= 5;
    type fsmd_state_type is (idle, delay);
    signal state_reg, state_next: fsmd_state_type;
    signal c_reg, c_next: unsigned(3 downto 0);
begin
    -- state and data registers
    process(clk,reset)
    begin
        if (reset='1') then
            state_reg <= idle;
            c_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            state_reg <= state_next;
            c_reg <= c_next;
        end if;
    end process;
end fsmd_arch;

```

RTL Hardware Design
by P. Chu

Chapter 12

17

```

-- next-state logic & data path functional units/routing
process(state_reg,go,stop,c_reg)
begin
    pulse <= '0';
    c_next <= c_reg;
    case state_reg is
        when idle =>
            if go='1' then
                state_next <= delay;
            else
                state_next <= idle;
            end if;
            c_next <= (others=>'0');
        when delay =>
            if stop='1' then
                state_next <= idle;
            else
                if (c_reg=P_WIDTH-1) then
                    state_next <= idle;
                else
                    state_next <= delay;
                    c_next <= c_reg + 1;
                end if;
            end if;
            pulse <= '1';
        end case;
    end process;
end fsmd_arch;

```


RTL Hardware Design
by P. Chu

Chapter 12

18

- Comparison:
 - FSM is most flexible and easy to comprehend
- What happens to the following modifications
 - The delay extend from 5 cycles to 100 cycles
 - The stop signal is only effective for the first 2 delay cycles and will be ignored otherwise

 - Can be easily extended in ASMD chart
- How about FSM and regular sequential circuit?



2. GCD circuit

- GCD: Greatest Common Divisor
 - E.g, gcd(1, 10)=1, gcd(12,9)=3
- GCD without division:

$$\text{gcd}(a, b) = \begin{cases} a & \text{if } a = b \\ \text{gcd}(a - b, b) & \text{if } a > b \\ \text{gcd}(a, b - a) & \text{if } a < b \end{cases}$$

- Pseudo algorithm

```

a = a_in;
b = b_in;
while (a != b) {
    if (b > a) then
        a = a - b;
    else
        b = b - a;
    end if
}
r = a;

```

- Modified pseudo algorithm w/o while loop

```

a = a_in;
b = b_in;
swap: if (a = b) then
    goto stop;
else
    if (b > a) then — swap a and b
        a = b;
        b = a;
    end if;
    a = a - b;
    goto swap;
end if;
stop: r = a;

```

-
- ```

graph TD
 Start(()) --> Do[do]
 Do --> Ready[ready ← 1]
 Ready --> LoopStart(())
 LoopStart --> DivT{div = 1}
 DivT -- F --> Ready
 DivT -- T --> Calc[$a \leftarrow a - b$
 $b \leftarrow b - a$]
 Calc --> DivT

```

25

- ```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity gcd is
    port(
        clk, reset: in std_logic;
        start: in std_logic;
        a_in, b_in: in std_logic_vector(7 downto 0);
        ready: out std_logic;
        r: out std_logic_vector(7 downto 0)
    );
end gcd ;

architecture slow_arch of gcd is
    type state_type is (idle, swap, sub);
    signal state_reg, state_next: state_type;
    signal a_reg, a_next, b_reg, b_next: unsigned(7 downto 0);


```

26

27

28

- $$\gcd(a, b) = \begin{cases} a & \text{if } a = b \\ 2\gcd(\frac{a}{2}, \frac{b}{2}) & \text{if } a \neq b \text{ and } a, b \text{ even} \\ \gcd(a, \frac{b}{2}) & \text{if } a \neq b \text{ and } a \text{ odd, } b \text{ even} \\ \gcd(\frac{a}{2}, b) & \text{if } a \neq b \text{ and } a \text{ even, } b \text{ odd} \\ \gcd(a-b, b) & \text{if } a > b \text{ and } a, b \text{ odd} \\ \gcd(a, b-a) & \text{if } a < b \text{ and } a, b \text{ odd} \end{cases}$$

 

30

- What is the performance now?
- Can we do better with more hardware resources

Square root approximation circuit

- A example of data-oriented (computation-intensive) application
- Equation:

$$\sqrt{a^2 + b^2} \approx \max((x - 0.125x) + 0.5y, x)$$

where $x = \max(|a|, |b|)$ and $y = \min(|a|, |b|)$

- 0.125x and 0.5y corresponds to shift right 3 bits and 1 bit

- Pseudo code:

```

a = a_in;
b = b_in;
t1 = abs(a);
t2 = abs(b);
x = max(t1, t2);
y = min(t1, t2);
t3 = x*0.125;
t4 = y*0.5;
t5 = x - t3;
t6 = t4 + t5;
t7 = max(t6, x)
r = t7;

```

- Direct “data-flow” implementation

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity sqrt is
    port(
        a_in, b_in: in std_logic_vector(7 downto 0);
        r: out std_logic_vector(8 downto 0)
    );
end sqrt;

architecture comb_arch of sqrt is
    constant WIDTH: natural:=8;
    signal a, b, x, y: signed(WIDTH downto 0);
    signal t1, t2, t3, t4, t5, t6, t7: signed(WIDTH downto 0);

```


```

begin
    a <= signed(a_in(WIDTH-1) & a_in); -- signed extension
    b <= signed(b_in(WIDTH-1) & b_in);
    t1 <= a when a > 0 else
        0 - a;
    t2 <= b when b > 0 else
        0 - b;
    x <= t1 when t1 - t2 > 0 else
        t2;
    y <= t2 when t1 - t2 > 0 else
        t1;
    t3 <= "000" & x(WIDTH downto 3);
    t4 <= "0" & y(WIDTH downto 1);
    t5 <= x - t3;
    t6 <= t4 + t5;
    t7 <= t6 when t6 - x > 0 else
        x;
    r <= std_logic_vector(t7);
end comb_arch;

```


- Requires one adder and six subtractors
- Code contains only concurrent signal assignment statements
- The order is not important.
- Sequence of execution is embedded in the flow of data

 - Data flow graph
 - Shows data dependency
 - Node (circle): an operation
 - Arches: input and output variables
- Note that there is limited degree of parallelism
 - At most two operations can be performed simultaneously




- RT methodology can be used to share the operator
- Tasks in converting a dataflow graph to an ASMD chart
 - Scheduling: *when* a function (circle) can start execution
 - Binding: *which* functional unit is assigned to perform the operation
- In square root algorithm,
 - all operations can be performed by a modified addition unit
 - No function unit is needed for shifting


- Scheduling with two functional units

 



- Scheduling with one functional unit

 

- ASMD chart

 

  - Registers can be shared as well
 - reduce the number of unique variables
 - A variable can be reused if its value is no longer needed
- E.g.,
 - Use r1 to replace a, t1 and y.
 - Use r2 to replace b, t2 and x.
 - Use r3 to replace t5, t6 and t7.



• VHDL code

- Needs to manually code the data path two insure functional units sharing
- One unit for abs and min
- One unit for abs, min, - and +
- Can be implemented by using an adder/subtractor with special input and output routing circuits

```

-- state & data registers
process(clk,reset)
begin
    if reset='1' then
        state_reg <= idle;
        r1_reg <= (others=>'0');
        r2_reg <= (others=>'0');
        r3_reg <= (others=>'0');
    elsif (clk'event and clk='1') then
        state_reg <= state_next;
        r1_reg <= r1_next;
        r2_reg <= r2_next;
        r3_reg <= r3_next;
    end if;
end process;

```

```

case state_reg is
    when idle =>
        if start='1' then
            r1_next <= signed(a_in(WIDTH-1) & a_in);
            r2_next <= signed(b_in(WIDTH-1) & b_in);
            state_next <= s1;
        else
            state_next <= idle;
        end if;
        ready <='1';
    when s1 =>
        r1_next <= au1_out; -- t1=|a|
        r2_next <= au2_out; -- t2=|b|
        state_next <= s2;
    when s2 =>
        r1_next <= au1_out; -- y=min(t1,t2)
        r2_next <= au2_out; -- x=max(t1,t2)
        state_next <= s3;
    when s3 =>
        r3_next <= au2_out; -- t5=x-0.125x
        state_next <= s4;
    when s4 =>
        r3_next <= au2_out; -- t6=0.5y+t5
        state_next <= s5;
    when s5 =>
        r3_next <= au2_out; -- t7=max(t6,x)
        state_next <= idle;
end case;

```

```

-- arithmetic unit 1
-- subtractor
diff <= sub_op0 - sub_op1;
-- input routing
process(state_reg,r1_reg,r2_reg)
begin
    case state_reg is
        when s1 => -- 0-a
            sub_op0 <= (others=>'0');
            sub_op1 <= r1_reg; -- a
        when others => -- s2: t2-t1
            sub_op0 <= r2_reg; -- t2
            sub_op1 <= r1_reg; -- t1
        end case;
    end process;

```

```

-- output routing
process(state_reg,r1_reg,r2_reg,diff)
begin
    case state_reg is
        when s1 => -- |a|
            if diff(WIDTH)='0' then -- (0-a)>0
                au1_out <= diff; -- -a
            else
                au1_out <= r1_reg; -- a
            end if;
        when others => -- s2: min(a,b)
            if diff(WIDTH)='0' then -- (t2-t1)>0
                au1_out <= r1_reg; -- t1
            else
                au1_out <= r2_reg; -- t2
            end if;
        end case;
    end process;

```

High-level synthesis

- Convert a “dataflow code” into ASMD based code (RTL code).
 - RTL code can be optimized for performance (min # clock cycles), area (min # functional units) etc.
 - Perform scheduling, binding
 - Minimize # registers and muxes
- Mainly for computation intensive applications (e.g., DSP)