
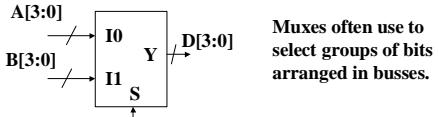


## Combinational Building Blocks

### 2/1 Multiplexor (MUX)

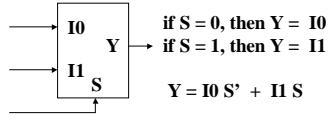


BR 8/99

1
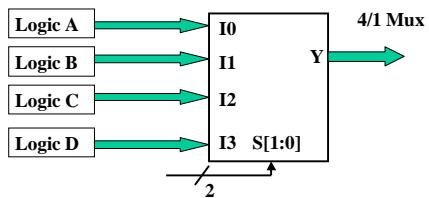
## What Good are Muxes ??

Sometimes want to have a bus be driven from multiple blocks, where only one block is driving the bus at a time.




N to 1 mux will select 1 source; Select bus needs to be  $\log_2(N)$ . Note that only ONE input can be selected at a time!

BR 8/99

2

## Higher Order Muxes

### 4/1 Mux

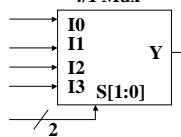


if  $S = "00"$ , then  $Y = I_0$   
if  $S = "01"$ , then  $Y = I_1$   
if  $S = "10"$ , then  $Y = I_2$   
if  $S = "11"$ , then  $Y = I_3$

$$Y = I_0 S_1' S_0' + I_1 S_1' S_0 + I_2 S_1 S_0' + I_3 S_1 S_0$$

BR 8/99

3

### 8/1 Mux

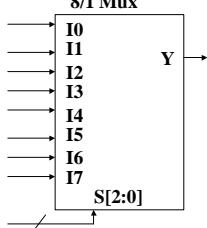


---

---

---

---

---

---

---

---



---

---

---

---

---

---

---

---



---

---

---

---

---


---

---

---

## Logic for 2/1, 4/1 Muxes


$$Y = I0 S' + I1 S$$

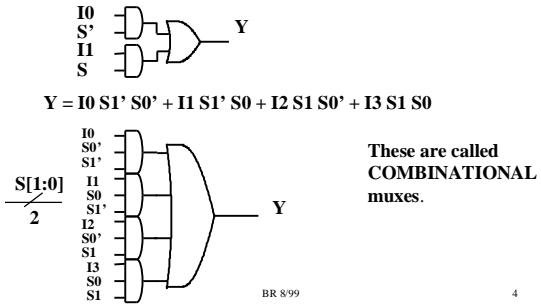

4
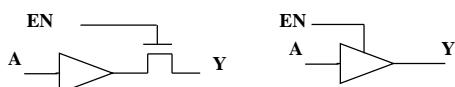
## Tri State Buffer

There is another way to drive a line or bus from multiple sources. Use a TRISTATE buffer.



When EN = 1, then  $Y = A$ .

When EN = 0, then  $Y = ??????$

Y is undriven, this is called the **high impedance state**.

Designate high impedance by a 'Z'.


When EN = 0, then  $Y = Z$  (high impedance)

BR 8/99

5
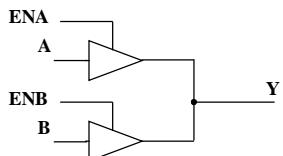
## Using TriState Buffers

Can use tristate buffers instead of a combinational 2/1 mux




Must make sure that ENA, ENB are not both '1' at same time, or Y will be driven from multiple sources

BR 8/99

6

### Using TriState Buffers (cont)

Only A or B is enabled at a time.

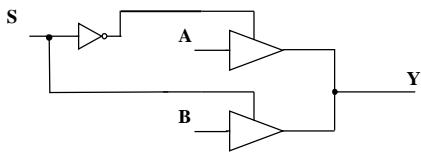

Implements 2/1 Mux function

If  $S=0$  then  $Y = A$   
If  $S=1$  then  $Y = B$

BR 8/99

7

---

---

---


---

---

---

---

### Using TriState Buffers (cont)

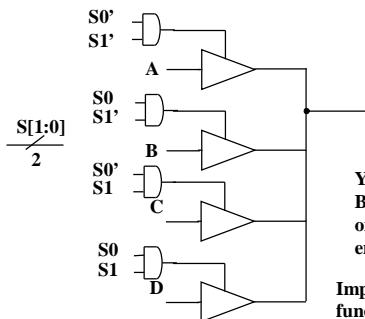

$Y$  is driven by A,  
B, C or D; only  
one source is  
enabled at a time.  
Implements 4/1 MUX  
function.

BR 8/99

8

---

---

---

---

---


---

---


### Decoders

Logic common to both of the previous mux implementations was the *decoder* function.

1 to 2 decoder

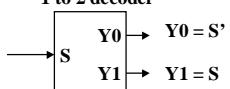

2 to 4 decoder

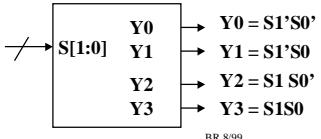

BR 8/99

9

---

---

---

---

---

---

---


---

---

---

---


Logic for 4/1 Combinational Mux

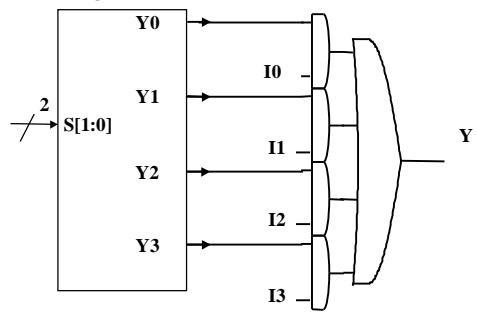

BR 8/99

10


4/1 Mux using Decoder + TSBs

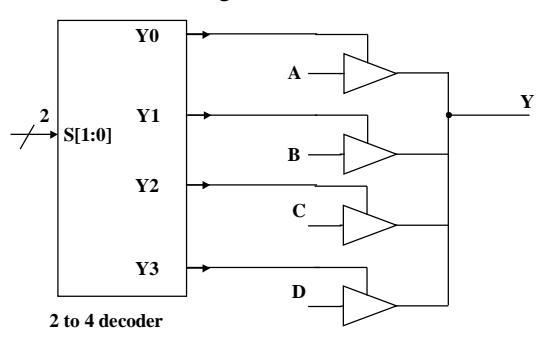

BR 8/99




11

3 to 8 Decoder

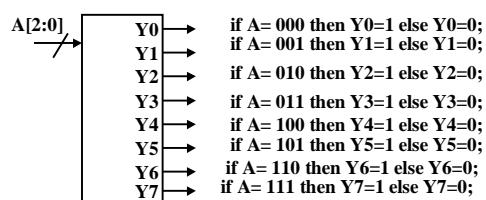


BR 8/99

12

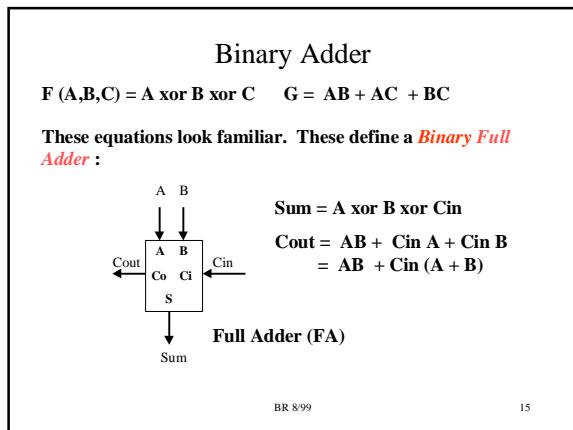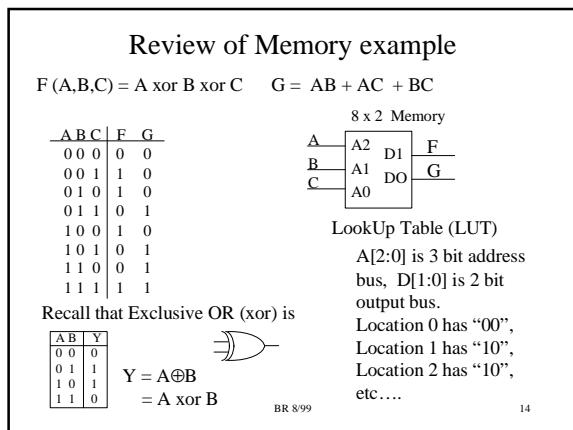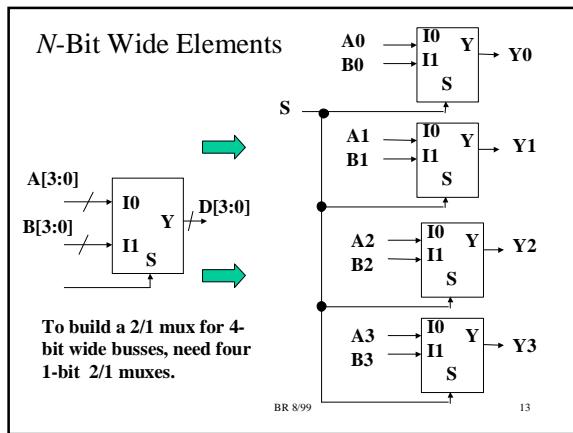


### 4 Bit Ripple Carry Adder

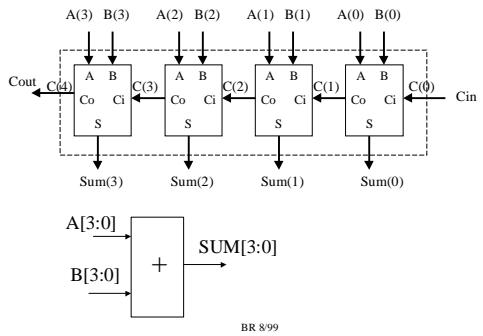

16

### Incrementer

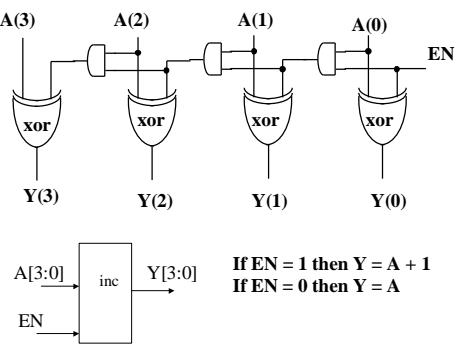

17

### What do You have to know?

- Structures for Muxes, Decoders, Ripple Carry adder, Incrementer
- What a tristate buffer is
- How to build muxes from all combinational logic or from combinational logic + tristate buffers
- Bus naming convention
- How to build N-bit wide elements from 1-bit wide elements

BR 8/99

18