

The Concept of a *Fault*

- Testing centers around detection of *faults* in a circuit.
- The digital world is made up of interconnected gates
 - Thus, only two things can fail - gates and their interconnections
- A faulty gate fails to perform its function correctly
- A faulty interconnection produces a “stuck at 1”, “stuck at 0”, or permanently tri-stated input.
- Problem: can you set up experiments that produce one result if the gate/interconnect is good, and another if it is bad?
- This leads to two closely related concepts.

Notes adapted from Prof Sam Rains

BR 1/99

1

Observability and Controllability


- Observability is the ability to observe a gate output directly at external pins
- Controllability is the ability to apply any and all desired inputs to a gate via external pins
- Test a gate completely, all combinations of inputs must be applied and the output corresponding to each input must be observed

Notes adapted from Prof Sam Rains

BR 1/99

2

Controllability: An Example

 


- How do you control the inputs to gate 2? Gate 3?
 - Gate 2: Set input A to 1 and apply four possible input combinations to inputs B, C (Sensitize Gate 1 to changes on B).
 - Gate 3: Set input A or B to 1 and apply all four possible input combinations to C, D (Sensitize Gate 2 to changes on C)

Notes adapted from Prof Sam Rains

BR 1/99

3

Observability: An Example

 

- How do you observe gate 1's output? Gate 2?
 - Gate 1: Set input C to 1 and D to 0 (Set Gates 2 and 3 so that they pass output A)
 - Gate 2: Set input D to 0

Notes adapted from Prof Sam Rains

BR 1/99

4

Extending the Concept

- A set of inputs and outputs designed to test a specific gate is called a *test vector*.
- A collection of inputs designed to test a specific gate or area completely is called a *test vector suite*.
- Once a test vector suite is developed for a block, you need to develop a way to get those inputs to the block and directly observe the block's outputs

Notes adapted from Prof Sam Rains

BR 1/99

5

Some Problems

- #1: Four additional test vectors are required for every additional 2-input gate. The number of test vectors increases as the number of gates increases.
- #2: The number of gates is increasing much faster than the number of inputs/outputs. This is making both controllability and observability more difficult.
- #3: Sequential circuits can be notoriously difficult to test. For example, a 16-bit counter has to be cycled through its entire count for complete testing.
- Some strategies have emerged to deal with these problems.


Notes adapted from Prof Sam Rains

BR 1/99

6

Automated Test Vector Generation

 - Software exists to analyze a digital design and perform the following functions:
 - Answer the question “What percentage of gates have been completely tested by the test vectors applied to the device?” This is known as **Fault Coverage**.
 - Generate test vectors to cover the remaining gates
- Fault Coverage curves look like:



Notes adopted from Prof Sam Rana

BR 1/99

7

Issues in Test Vector Generation

- Issue #1: Diminishing Returns -- Vectors start covering smaller and smaller fractions of the device
- Issues #2: Some tests may be nearly impossible or truly impossible (non-testable faults)
- Without extra hardware added explicitly to help with testing, fault coverage is typically in the 90% to 95% range.

Notes adopted from Prof Sam Rana

BR 1/99

8

Built-In Self Test (BIST)

- One way to add reliability to a component or part of a chip is with Built-In Self Test (BIST)
- An example is the Motorola 68030 MCU
 - Motorola has added a small set of instructions which they certify tests a significant fraction of the 68030's gates.
 - Can be incorporated into the low level startup process to detect and processor faults.

Notes adopted from Prof Sam Rana

BR 1/99

9

BIST Approach

- Add circuitry so that on powerup a small ROM or pseudo-random sequence generator applies a series of inputs
- The outputs are tested for a correct answer, usually by accumulating the outputs into a checksum value (either by XOR or Cyclic Redundancy Check - CRC)
- The pseudo random pattern generation and checksum accumulation does not need many gates
- The probability of passing self-test with an undiagnosed fault can be made small (depends on number of patterns).


Notes adopted from Prof Sam Rana

BR 1/99

10

Linear Feedback Shift Register (LFSR)

 A Linear Feedback Shift Register can be used a pseudo-random sequence which can be used as test vectors for design.



For a 16 bit register,

$$\text{LSB} = \text{dout}(1) \text{ xor } \text{dout}(2) \text{ xor } \text{dout}(4) \text{ xor } \text{dout}(15)$$

Notes adopted from Prof Sam Rana

BR 1/99

11

LFSR (cont)


- For an N-bit shift register, the maximum length sequence that can be generated is $2^N - 1$ (sequence will repeat after this number of shifts).
 - For 8 bits, will generate 255 out of the possible 256 values.
- Assuming a reset value of '0' for the shift register, the missing code will be 255 for the following feedback combinations:
 - $\text{Lsb} = 1 \text{ xor } b(1) \text{ xor } b(2) \text{ xor } b(3) \text{ xor } b(7)$
 - $\text{Lsb} = 1 \text{ xor } b(3) \text{ xor } b(4) \text{ xor } b(5) \text{ xor } b(7)$
 - $\text{Lsb} = 1 \text{ xor } b(2) \text{ xor } b(4) \text{ xor } b(6) \text{ xor } b(7)$
- Each of the above feedback arrangements produces a different sequence.

Notes adopted from Prof Sam Rana

BR 1/99

12

Built in Self Test (BIST)

 

DUT = device under test

When in self test, inputs to DUT is taken from LFSR and checksum register accumulates the output. After some X number of test vectors have been applied, compare check sum output against a golden value – if the same, then system has passed self test.


Notes adapted from Prof Sam Rana

BR 1/99

13

Is Fault Coverage Sufficient Without Extra Hardware?

 - Consider study results that show defect level vs. fault coverage



Source: 1980 study by Delco and Motorola, as cited in TI's IEEE 1149.1 Testability Primer

To get a single chip defect rate of 100 defective parts per million parts, you need 99.9% fault coverage! Do you really need a defect rate of less than 100 ppm?


Notes adapted from Prof Sam Rana

BR 1/99

14

The Effects of Single Chip Defects

 - Consider the effects of having multiple chips on a board



Source: TI's IEEE 1149.1 Testability Primer

If you have 5 ASIC's on a board, you need to have around 60 ppm defective ASIC's to achieve 300 ppm defective boards.

Notes adapted from Prof Sam Rana

BR 1/99

15

What does all this mean?

- You need fault coverage in the 99% to 99.9% range
- You need automated test vector generation and fault grading tools
 - Fault grading tells you % fault coverage for a test vector suite
- You need extra hardware to improve testability.


Notes adapted from Prof Sam Rana

BR 1/99

16

A Solution: Scan Paths

 - Is there a way to apply inputs directly to gates and observer outputs directly?
- Yes - with a *Scan Path*. A Scan Path ties all FFs in your design into a shift register.
 - Requires Scannable DFFs




Notes adapted from Prof Sam Rana

BR 1/99

17

A Scan Path

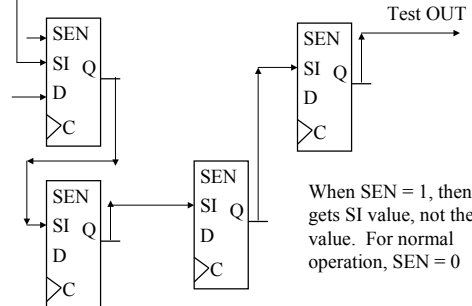

When SEN = 1, then DFF gets SI value, not the D value. For normal operation, SEN = 0

Notes adapted from Prof Sam Rana

BR 1/99

18

Scan Path Operation

- Assume ALL FFs in design are in tied into a Scan Path and let there be N FFs.
- Apply $SEN = '1'$, and clock test vector serially into scan path. Will take N clocks.
- Apply, $SEN = '0'$, and clock ONCE. This will test the design using the test vector!
- Apply $SEN = '1'$, and clock in next test vector. At same time, you clocking OUT the result of the last test vector!!!
- After first test vector, each test vector takes $N+1$ clocks!!

BR 1/99

19

Notes adapted from Prof Sam Ravi

19



20

Introducing IEEE 1149.1 (JTAG)

- In order to standardize scan path design and support, the Joint Test Action Group, comprised of over 200 electronics companies, developed an industry-wide standard for scan path support
- It has been adopted as IEEE Standard 1149.1
- It is usually called “the JTAG port” in sales literature (or Boundary Scan)
- Every JTAG compatible port can be chained together to form a serial device
- Can be used to support fault detection at the single chip level, detection of board level faults, and even some PLDs/FPGAs can be programmed with it.

Notes adopted from Prof Sam Rains

BR 1/99

21

- Notes adopted from Prof Sam Russ

21

Basics of JTAG

- The JTAG standard adds four signals to every compatible device
 - TCK: a clock signal for the test port
 - TMS: Test Mode Select - determines whether or not the scan path is active and controls the mode it is in.
 - TDI: Test Data In - serial data input
 - TDO: Test Data Out - serial data output
- The standard also specifies some standard operating modes
- For example, the the serial shift register can be set to bypass the chip, making access to other chips faster.
- Vendor specific commands be added.

Notes adapted from Prof Sam Rains

BR 1/99

22

- Notes adopted from Prof Sam Russell

22



23



24

Some Keys to an Effective Test Strategy

- Decide early, not late, on test strategy
 - Other test approaches beside BIST, JTAG
- Identify software tools for test vector generation, fault grading
- Have to plan test strategy through development, prototyping, manufacturing, and maintenance
- Adding a JTAG bus to a board (and JTAG compatible components) can be a cost effective way of adding a large amount of testability to your design

Summary

- The purpose of testing is to uncover faults in a system (chip or board)
- Faults are found by applying test vectors and observing results
- Test vectors can be generated manually or automatically
- Usually have to add extra hardware to improve testability.
- Scan paths can increase chip and board level testability.
- JTAG adds four pins and supports a variety of test modes; almost all electronics vendors support JTAG.