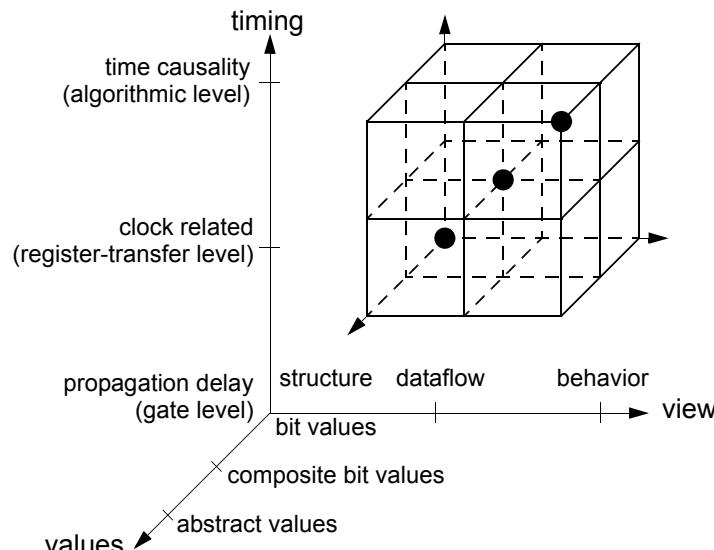





HDL Design Cube



Synthesis and VHDL

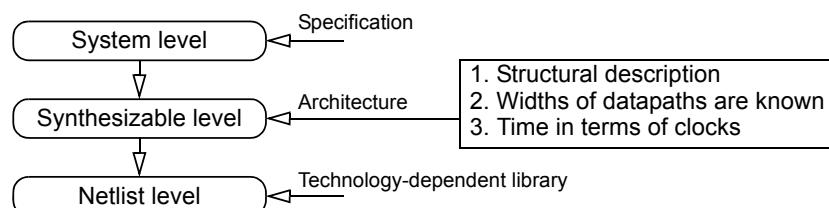- VHDL LRM defines only simulation semantics of the language.
- LRM – Language Reference Manual



- **Synthesis restrictions:**
 - the lack of maturity of synthesis tools
 - the state-of-art in synthesis targets RTL synthesis only
 - certain VHDL features are simply not synthesizable
- **The same applies to Verilog...**



Synthesis style

- Delay expressions (after clauses, wait for statements are ignored)
- Certain restrictions on the writing of process statement occur
- Only a few types are allowed
 - integer, enumerated, e.g., bit, bit_vector, signed
- Type conversion and resolution functions are not interpreted
- Description is oriented towards synchronous styles with explicit clocks
- Types: enumeration, integer, one-dimensional array, record

```
type WORD is array (31 downto 0) of BIT;
type RAM is array (1023 downto 0) of WORD;
```
- In record, an item address becomes hardware coded
- !!! Time type is not supported !!!
- No explicit or default initialization
- Parenthesis in expressions have effect on HW generation
- Some arithmetic operations are supported partially only



Sensitivity list

- Equivalent processes:

```
process (A, B, C)
...
begin
...
end process;
```

==

```
process
...
begin
wait on A, B, C;
...
end process;
```

~~


```
process
...
begin
...
wait on A, B, C;
end process;
```

- Some synthesizers support only sensitivity list for combinational logic
- In case of single synchronization process there is no need to “remember” at which synchronization point it was stopped -> such behavior does not imply memorization
- Process with multiple synchronization points, i.e. several wait states, infer memorization – FSM




Assignment statement synthesis
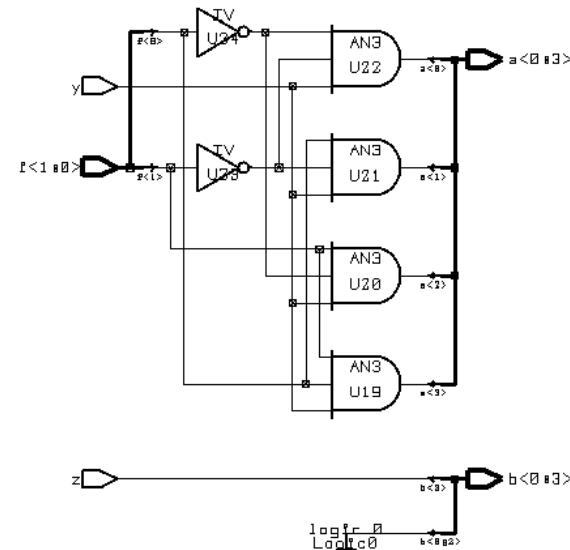
```
signal A,B: BIT_VECTOR(0 to 3);
signal I: INTEGER range 0 to 3;
signal Y,Z: BIT;
-- . .
process ( I, Y, Z ) begin
  A<="0000";
  B<="0000";
  A(I)<=Y; -- Computable index
  B(3)<=Z; -- Constant index
end process;
```





if statement synthesis
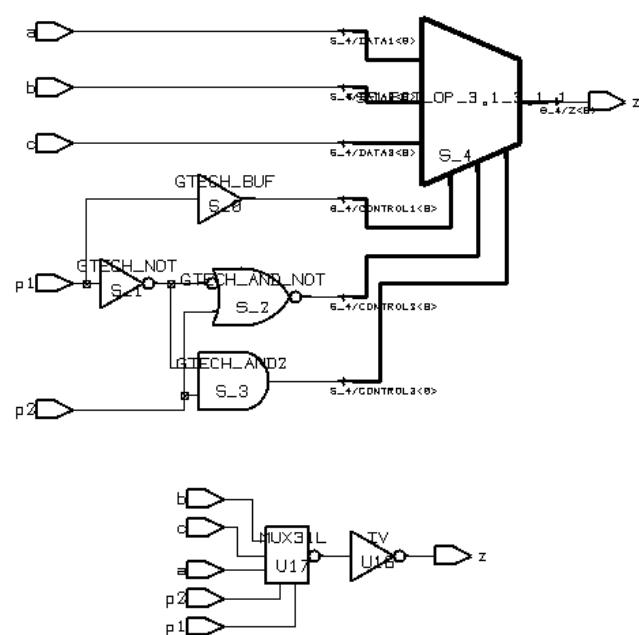
```
signal A,B,C,P1,P2,Z: BIT;
-- . .
process (P1,P2,A,B,C) begin
  if (P1 = '1') then
    Z <= A;
  elsif (P2 = '0') then
    Z <= B;
  else
    Z <= C;
  end if;
end process;
```





SR latch

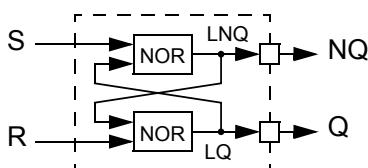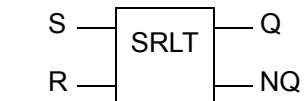

```
use WORK.CHECK_PKG.all;
entity SRLT is
  port ( S, R:  in bit;
         Q, NQ: out bit );
begin
  NOT_AT_THE_SAME_TIME(S,R);
end SRLT;

architecture A1 of SRLT is
  signal LQ:  bit := '1';
  signal LNQ: bit := '0';
begin
  LNQ <= S nor LQ;
  LQ  <= R nor LNQ;
  Q   <= LQ;
  NQ  <= LNQ;
end A1;
```

- **NB! Asynchronous feed-back is temporarily cut by synthesizers...**



Combinational circuit

- **A process is combinational, i.e. does not infer memorization, if:**
 - the process has an explicit sensitivity list or contains a single synchronization point (waiting for changes on all input values);¹⁾
 - no local variable declarations, or variables are assigned before being read;
 - all signals, which values are read, are part of the sensitivity list;²⁾ and
 - all output signals are targets of signal assignments independent on the branch of the process, i.e. all signal assignments are covered by all conditional combinations.

¹⁾ waiting on a clock signal, e.g., “wait on clk until clk='1'; ”, implies buffered outputs (FF-s)



²⁾ interpretation may differ from tool to tool

Complex assignments

- No memory:

```
S <= A when X='1' else B when Y='1' else C;
```

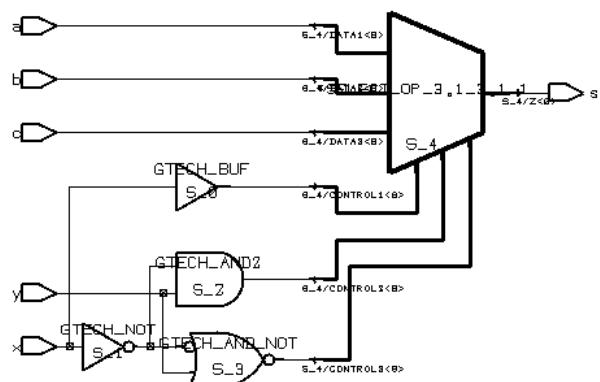
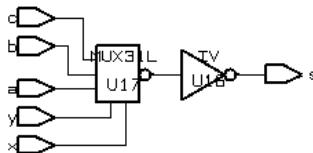
```
process (A, B, C, X, Y) begin
    if      X='1' then S <= A;
    elsif   Y='1' then S <= B;
    else          S <= C;
    end if;
end process;
```



Complex assignments

- Memory element generated:
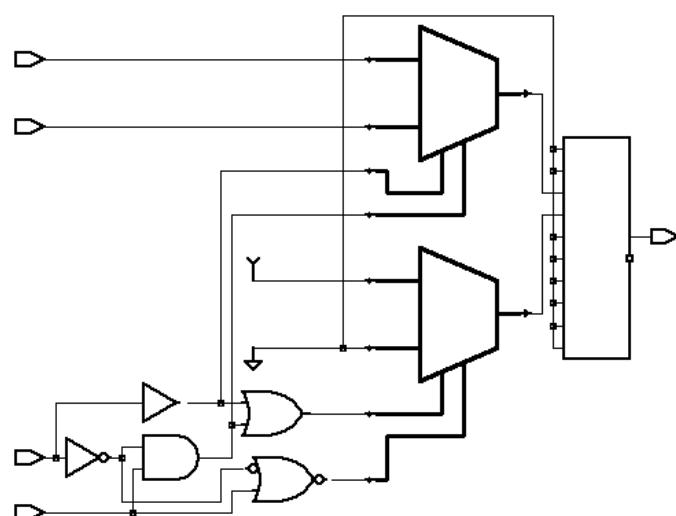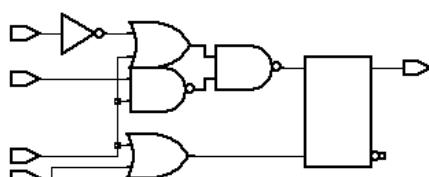
```
process (A, B, X, Y) begin
    if      X='1' then S <= A;
    elsif   Y='1' then S <= B;
    end if;
end process;
```







Complex assignments

- Memory element generated (#2):

```
S <= A when X='1' else B when Y='1' else S;
```
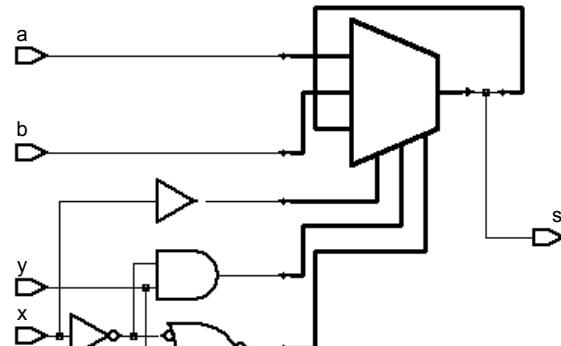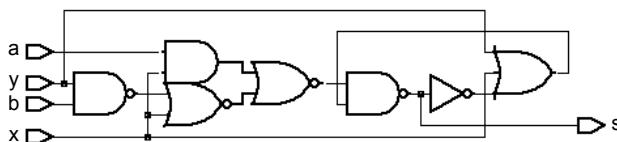
```
process (A, B, X, Y) begin
    if      X='1' then    S <= A;
    elsif  Y='1' then    S <= B;
    else                  S <= S;
    end if;
end process;
```




Flip-flops

- Process

```
P1_FF: process (CLK)
begin
    if CLK='1' and CLK'event then
        Q<=D;
    end if;
end process P1_FF;

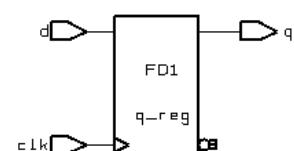
P2_FF: process
begin
    wait on CLK until CLK='1';
    Q<=D;
end process P2_FF;
```





Latch vs. Flip-flop?

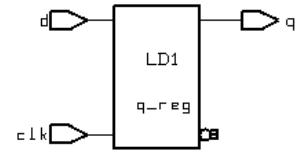
```
P1_L: process (CLK, D) begin
    if CLK='1' then      Q <= D;
    end if;
end process P1_L;
```



```
P2_FL: process (CLK) begin
    if CLK='1' then      Q<=D;
    end if;
end process P2_FL;
```

- Simulation OK but not synthesis!
- Warning: Variable 'd' is being read
-- in routine .. line .. in file '...',
-- but is not in the process sensitivity
-- list of the block which begins
-- there. (HDL-179)
- Result - latch

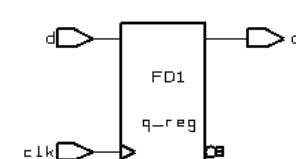
```
P1_FF: process (CLK) begin
    if CLK='1' and
        CLK'event then  Q<=D;
    end if;
end process P1_FF;
```



Flip-flops

- Process + reset & enable
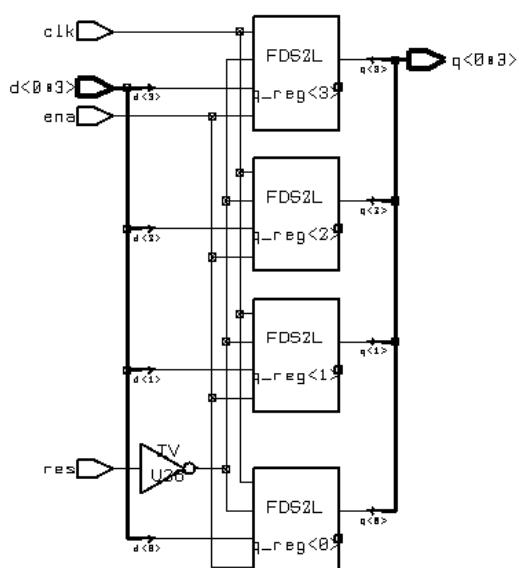
```
P3_FF: process (CLK)
begin
    if CLK='1' and CLK'event then
        if      RES='1' then
            Q<=(others=>'0');
        elsif ENA='1' then
            Q<=D;
        end if;
    end if;
end process P3_FF;
```






Flip-flops


- Process + asynchronous reset & enable
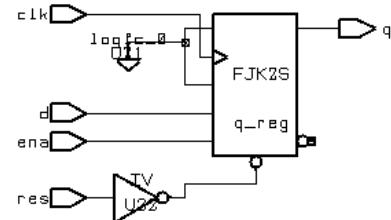
```
P4_FF: process (RES,CLK)
begin
    -- asynchronous reset
    if RES='1' then Q <= '0';
    elsif CLK='1' and CLK'EVENT then
        if ENA='1' then Q <= D;
        end if;
    end if;
end process P4_FF;
```



Synthesis rules

- Guidelines in priority order:
 - the target signal(s) will be synthesized as flip-flops when there is a signal edge expression, e.g. CLK'event and CLK='1', in the process
 - usually, only one edge expression is allowed per process
 - different processes can have different clocks (tool depending)
 - the target signal will infer three-state buffer(s) when it can be assigned a value 'Z'
 - example: Q <= D when SEL='1' else 'Z';
 - the target signal will infer a latch (latches) when the target signal is not assigned with a value in every conditional branch, and the edge expression is missing
 - a combinational circuit will be synthesized otherwise
- It is a good practice to isolate flip-flops, latches and three-state buffers inferences to ensure design correctness

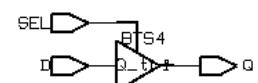





Signal versus variable

- The hardware resulting from synthesis of variables or signals differs: either nothing, wires, or memory elements

```
signal A1, A2: BIT;
-- . .
process (CLOCK)
    variable A3: BIT;
begin
    if CLOCK='1' and CLOCK'event then
        A3 := A1 and A2;
        Z <= A3;
    end if;
end process;

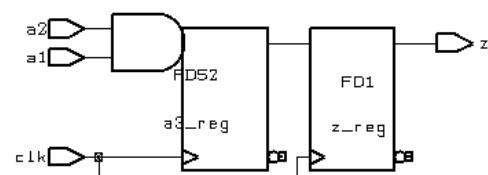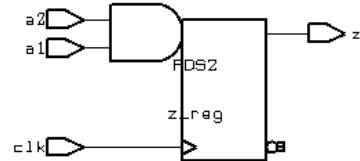signal A1, A2, A3: BIT;
-- . .
process (CLOCK)
begin
    if CLOCK='1' and CLOCK'event then
        A3 <= A1 and A2;
        Z <= A3;
    end if;
end process;
```



Arithmetics

- Overloaded arithmetic operations:

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
```
- Sources of the named packages are in the directory: \$SYNOPSYS/packages/IEEE/src
 - \$SYNOPSYS/packages is the root directory for all Synopsys packages
 - Be careful with '**', '/', '**' - extremely chip area consuming
 - Safe in some special cases - multiplication by power of two
- Use parenthesis to group a set of gates

Initial values


- The default values inherited from type or subtype definitions
- The explicit initialization that is given when the object is declared
- A value assigned using a statement at the beginning of a process
- Only the last case is supported by synthesis tools.
- Usually, a part of the synthesizable code is devoted to set/reset constructions

Don't care values and synthesis


```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
architecture C of DONT_CARE is
    signal SEL: STD_LOGIC_VECTOR(1 TO 3);
    signal A, B, X: STD_LOGIC;
begin
    process (A, B, SEL) begin
        case SEL is
            when "001" => X <= A;
            when "010" => X <= B;
            when others => X <= '-';
        end case;
    end process;
end C;

```

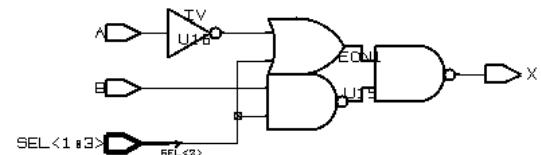

Data-part & control-part

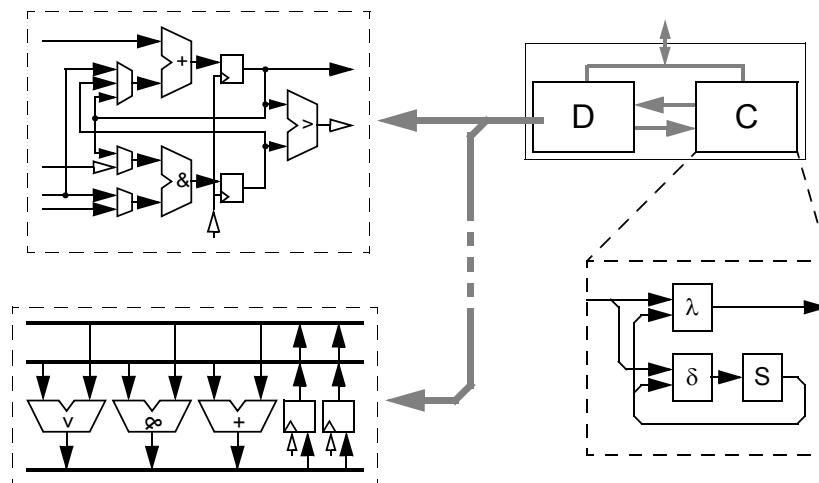


- one unit – one process
 - functional units – combinational processes [all inputs in the sensitivity list]
 - storage units – clocked processes [activation at clock edge]



FSM in VHDL

- **FSM:** $M = (S, I, O, \delta, \lambda)$
 - S : set of states
 - I : set on inputs
 - O : set of outputs
 - δ : transition function - $\delta: S \times I \rightarrow S$
 - λ : output function - $\lambda: S \times I \rightarrow O$
- **How many processes?**
 - Process per block
- **Three processes**
 - (1) transition function, (2) output function, (3) state register
- **Two processes**
 - (1) merged transition and output functions, (2) state register [Mealy]
- **One process**
 - buffered outputs! [Moore]

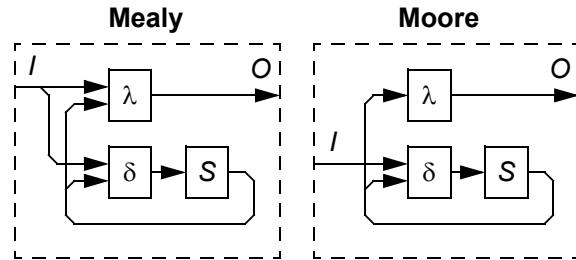

FSM as a single process

```
-- RESET is the asynchronous reset, CLK is the clock
-- STATE is a variable (or signal) memorizing the current state
process(RESET,CLK)
begin
    if RESET='1' then          -- asynchronous reset
        STATE <= S_INIT;
    elsif CLK='1' and CLK'EVENT then
        case STATE is
            when S_INIT => if I0='1' then STATE <= S5; end if;
            when ... => ...
        end case;
    end if;
end process;
```



Three process FSM

- storage elements, transition function & output function

```
architecture B of FSM is
    type TYPE_STATE is (S_INIT,S1,...Sn);
    signal CURRENT_STATE, NEXT_STATE : TYPE_STATE;
begin
    P_STATE: process begin -- sequential process
        wait until CLK'EVENT and CLK='1';
        if RESET ='1' then CURRENT_STATE <= S_INIT;
        else                  CURRENT_STATE <= NEXT_STATE; end if;
    end process P_STATE;
```

continue...



Three process FSM

```
P_NEXT_STATE: process (I0, ..., CURRENT_STATE) begin
    NEXT_STATE <= CURRENT_STATE;
    case CURRENT_STATE is
        when S_INIT => if I0='1' then NEXT_STATE <= S5; end if;
        when ... => ...
    end case;
end process P_NEXT_STATE;



P_OUTPUTS: process (CURRENT_STATE) begin
    case CURRENT_STATE is
        when S_INIT => O <= '0';
        when ... => ...
    end case;
end process P_OUTPUTS;
end B;
```



FSM #2 – description styles & synthesis

Two processes (modulo-4 counter)

```
library IEEE; use IEEE.std_logic_1164.all;
entity counter03 is
  port ( clk: in bit;
         resetn: in std_logic;
         three: out std_logic );
end entity counter03;
architecture fsm2 of counter03 is
  subtype state_type is integer range 0 to 3;
  signal pres_state, next_state: state_type := 0;
begin
  process (clk) begin -- State memory
    if clk'event and clk = '1' then
      pres_state <= next_state;
    end if;
  end process;
  -- Next state & output functions
  process (resetn, pres_state) begin
    three <= '0';
    if resetn='0' then    next_state <= 0;
    else
      case pres_state is
        when 0 to 2 => next_state <= pres_state + 1;
        when 3 => next_state <= 0;  three <= '1';
      end case;
    end if;
  end process;
end architecture fsm2;
```

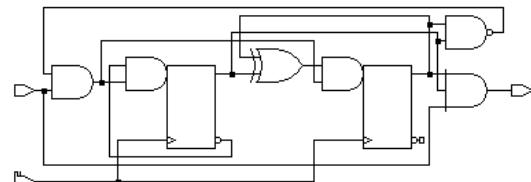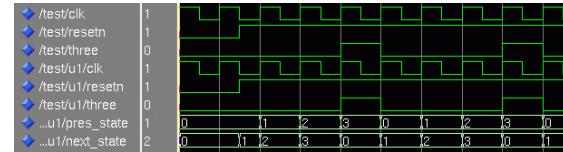

22 gates / 3.70 ns





FSM #2 – description styles & synthesis

Three processes (modulo-4 counter)

```
library IEEE; use IEEE.std_logic_1164.all;
architecture fsm3 of counter03 is
  subtype state_type is integer range 0 to 3;
  signal pres_state, next_state: state_type := 0;
begin
  process (clk) begin -- State memory
    if clk'event and clk = '1' then
      pres_state <= next_state;
    end if;
  end process;

  -- Next state function
  process (resetn, pres_state) begin
    if resetn='0' then    next_state <= 0;
    else
      if pres_state=3 then    next_state <= 0;
      else    next_state <= pres_state + 1;
      end if;
    end if;
  end process;
  -- Output function
  process (resetn, pres_state) begin
    if pres_state=3 then    three <= '1';
    else    three <= '0';
    end if;
  end process;
end architecture fsm3;
```

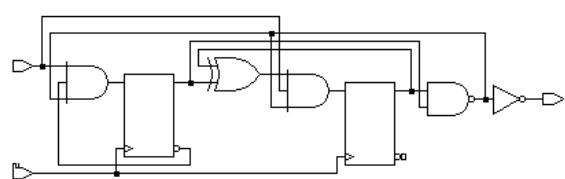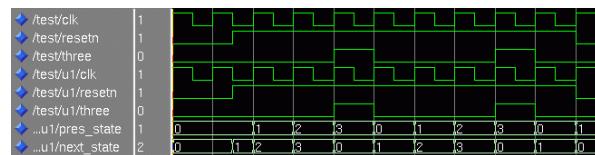

23 gates / 4.36 ns





FSM #2 – description styles & synthesis

One process (modulo-4 counter)

```
library IEEE; use IEEE.std_logic_1164.all;
architecture fsm1 of counter03 is
    subtype state_type is integer range 0 to 3;
    signal state: state_type := 0;
begin
    process (clk) begin
        if clk'event and clk = '1' then
            three <= '0';
            if resetn='0' then      state <= 0;
            else
                case state is
                    when 0 | 1 => state <= state + 1;
                    when 2 => state <= state + 1; three <= '1';
                    when 3 => state <= 0;
                end case;
            end if;
        end if;
    end process;
end architecture fsm1;

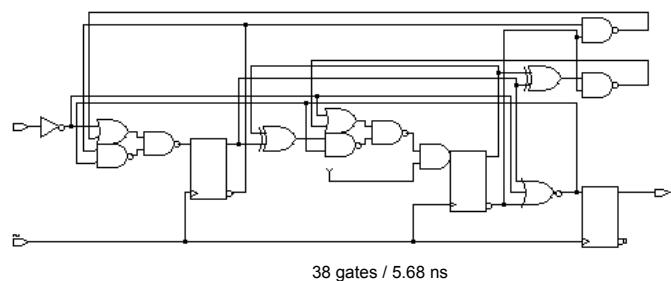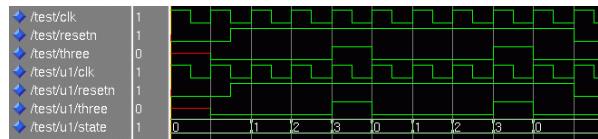// Another version to build the process
process begin
    wait on clk until clk='1';
    three <= '0';
    if resetn='0' then      state <= 0;
    else
        -- and so on...
    end if;
end process;
```



Using generics

```
entity AND_N is
    generic (N: POSITIVE);
    port      (DIN: in BIT_VECTOR(1 to N); R: out BIT);
end AND_N;

architecture A1 of AND_N is
    signal INTER: BIT_VECTOR(1 to N);
begin
    INTER(1) <= DIN(1);
    L: for I in 1 to N-1 generate
        INTER(I+1) <= DIN(I+1) and INTER(I);
    end generate;
    R <= INTER(N);
end A1;

C1: AND_N generic map (N=>12) port map(IN_DATA, OUT_DATA);
```



for-loop versus while-loop?

- **May be tool dependent!**

- Design Compiler (Synopsys): **for** - parallel, **while** - sequential
- Leonardo (Mentor Graphics): depending on the timing constructions

- **for-loop**

- parallel implementation
- no timing control (wait) in the loop body

```
for i in 0 to 7 loop
    x(i) := a(i) and b(i);
end loop;
```

- **while-loop**

- sequential implementation
- timing control (wait) required in the loop body

```
i := 0;
while i<7 loop
    data(i) := in_port;
    wait on clk until clk='1';
    i := i + 1;
end loop;
```



Multiple wait statements

- VHDL semantics must be preserved
 - different interpretations possible
- Distributing operations over multiple clock steps

- Algorithm

- Inputs: a, b, c, d
- Output: x
- Coefficients: c1, c2
- $x = a + b*c1 + c*c2 + d$
- Timing constraint - 3 clock periods

```
process
    variable av, bv, cv, dv: ...;
begin
    av:=a; bv:=b; cv:=c; dv:=d;
    wait on clk until clk='1';
    wait on clk until clk='1';
    x <= av + bv * c1 + cv * c2 + dv;
    wait on clk until clk='1';
end process;
```



Multiple wait statements

- Behavioral interpretation may lead to an unoptimal solution

```
process
  variable av, bv, cv, dv: ...;
begin
  av:=a; bv:=b; cv:=c; dv:=d;
  wait on clk until clk='1';
  wait on clk until clk='1';
  x <= av + bv * c1 + cv * c2 + dv;
  wait on clk until clk='1';
end process;
```

2 multipliers & 3 adders

```
process
  variable av, bv, cv, dv: ...;
  variable r1, r2: ...;
begin
  av:=a; bv:=b; cv:=c; dv:=d;
  r1 := av + dv;    r2 := bv * c1;
  wait on clk until clk='1';
  r1 := r1 + r2;   r2 := cv * c2;
  wait on clk until clk='1';
  x <= r1 + r2;
  wait on clk until clk='1';
end process;
```

Behavioral Synthesis
(High-Level Synthesis)

1 multiplier & 1 adder



Inserting wait statements


- VHDL semantics preserved for inputs/outputs
 - targeting as-fast-as-possible (AFAP) schedules
- 16-tap FIR filter
 - new input and output data at every rising flank of sys_clk (sampling clock)
 - internal clock can be added
- How to implement loops?
 - 1st - in parallel (shift-register)
 - 2nd - sequentially
 - multiply-and-accumulate (MAC)
 - ROM for coefficients

```
process
  variable sum: ...;
  variable buff: ...; -- array (0 to 15)
begin
  for i in 15 downto 1 loop
    buff(i) := buff(i-1);
  end loop;
  buff(0) := data_in;    sum := 0;
  for i in 0 to 15 loop
    sum := sum + buff(i) * coeff(i);
  end loop;
  x <= sum;
  wait on sys_clk until sys_clk='1';
end process;
```



Verilog – synthesis rules

- **Guidelines in priority order:**
 - the target signal(s) will be synthesized as flip-flops when there is a signal edge expression, e.g. “@(posedge CLK)”, in the behavioral statement
 - only one edge expression is allowed per behavioral statement
 - different statements can have different clocks (tool depending)
 - the target signal will infer three-state buffer(s) when it can be assigned a value ‘Z’
 - example: $q = sel == 1 ? d : 'bz;$
 - the target signal will infer a latch (latches) when the target signal is not assigned with a value in every conditional branch, and the edge expression is missing
 - a combinational circuit will be synthesized otherwise
- **It is a good practice to isolate flip-flops, latches and three-state buffers inferences to ensure design correctness**

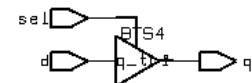

Combinational circuit

- **A process is combinational, i.e. does not infer memorization, if:**
 - the behavioral statement has a sensitivity list in the beginning (waiting for changes on all input values); ¹⁾
 - signals are assigned before being read;
 - all signals, which values are read, are part of the sensitivity list; ²⁾ and
 - all output signals are targets of signal assignments independent on the branch of the process, i.e. all signal assignments are covered by all conditional combinations.

¹⁾ waiting on a clock signal, e.g., “@(posedge clk)”, implies buffered outputs (FF-s)

²⁾ interpretation may differ from tool to tool

Sensitivity list

- Equivalent statements:

```
always
  @ (a or b or c or x or y)
begin
  if (x==1)      s=a;
  else if (y==1) s=b;
  else           s=c;
end
```

==

```
always begin
  @ (a or b or c or x or y);
  if (x==1)      s=a;
  else if (y==1) s=b;
  else           s=c;
end
```



- In case of single synchronization process there is no need to "remember" at which synchronization point it was stopped -> such behavior does not imply memorization

Complex assignments

- No memory:

```
assign s = x==1 ? a : y==1 ? b : c;
```

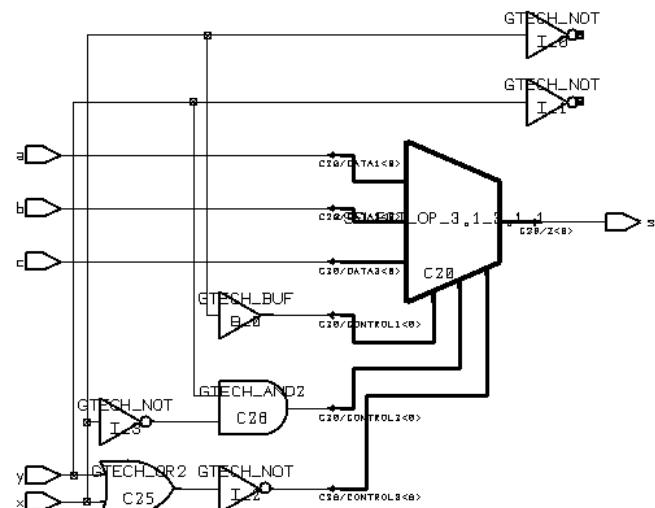
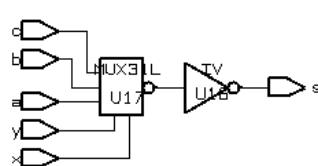
```
always
  @ (a or b or c or x or y)
  if (x==1)      s=a;
  else if (y==1) s=b;
  else           s=c;
```



Complex assignments

- Memory element generated:
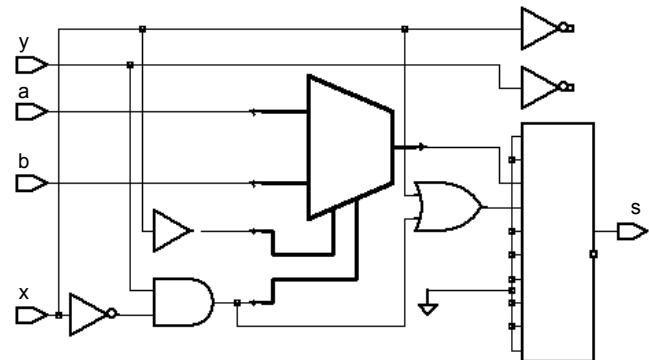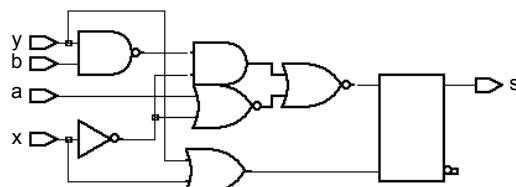
```
always begin
    @ (a or b or x or y);
    if (x==1)      s=a;
    else if (y==1) s=b;
end
```



Flip-flops


```
always @ (posedge clk) q = d;
```

```
always @ (posedge clk) q <= d;
```

- synchronous reset

```
always @ (posedge clk)
    if (res==1) q = 0;
    else        q = d;
```
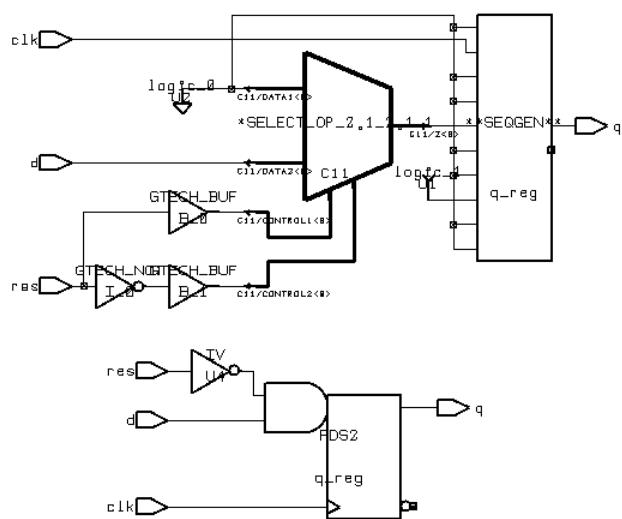
```
always begin
    @ (posedge clk);
    if (res==1) q = 0;
    else        q = d;
end
```






Flip-flops

- **asynchronous reset**

```
always
  @ (posedge res or
       posedge clk)
    if (res==1) q = 0;
    else         q = d;

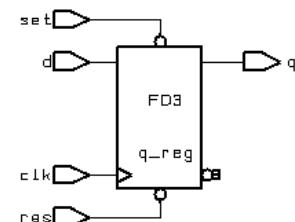
always
  @ (negedge res or
       negedge set or
       posedge clk)
    if (res==0)      q = 0;
    else if (set==0) q = 1;
    else             q = d;
```



Flip-flops

- **asynchronous reset - the order of signals!**

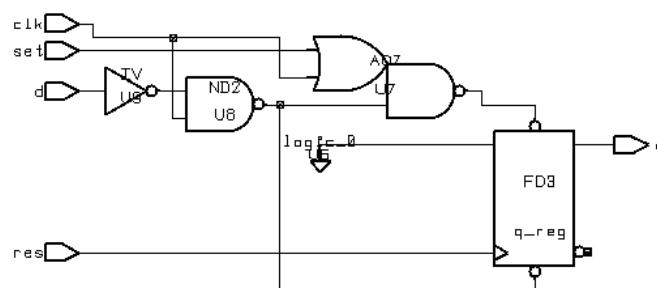
```
always @ (posedge res or posedge set or posedge clk)
  if (clk==1)      q = d;
  else if (set==1) q = 1;
  else             q = 0;
```



Blocking versus non-blocking

```
module sig_var_b (clk, a1, a2, z);
    input clk, a1, a2;
    output z; reg z; reg a3;
    always @(posedge clk) begin
        a3 = a1 & a2;
        z <= a3;
    end
endmodule // sig_var_b
```
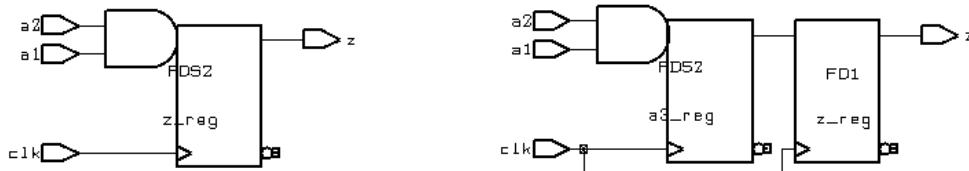
```
module sig_var_n (clk, a1, a2, z);
    input clk, a1, a2;
    output z; reg z; reg a3;
    always @ (posedge clk) begin
        a3 <= a1 & a2;
        z <= a3;
    end
endmodule // sig_var_n
```




Compare – signal versus variable in VHDL

```
process (CLK)
    variable A3 : BIT;
begin
    if CLK'event and CLK='1' then
        A3 := A1 and A2;
        Z <= A3;
    end if;
end process;
```

```
signal A3 : BIT;
-- ...
process (CLK) begin
    if CLK'event and CLK='1' then
        A3 <= A1 and A2;
        Z <= A3;
    end if;
end process;
```

Data-part, control-part & FSM

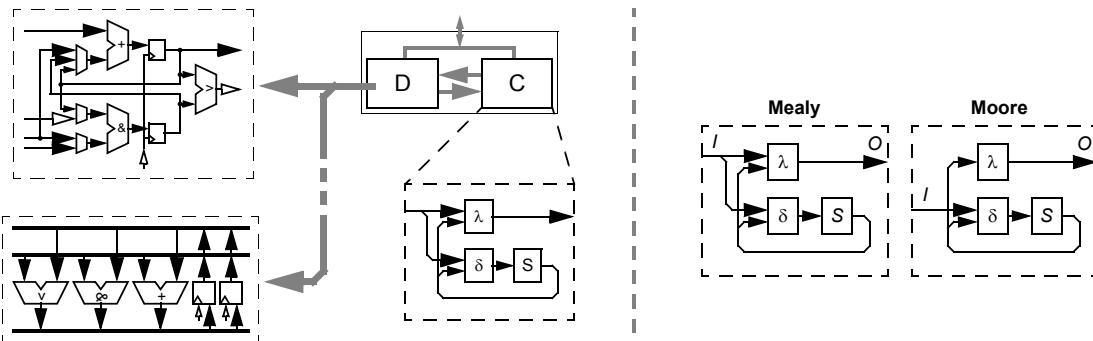


- one unit – one process
 - functional units – combinational processes [all inputs in the sensitivity list]
 - storage units – clocked processes [activation at clock edge]
- **FSM:** $M = (S, I, O, \delta, \lambda)$ – process per block
- Three processes – (1) transition function, (2) output function, (3) state register
- Two processes – (1) merged transition and output functions, (2) state register [Mealy]
- One process – buffered outputs! [Moore]


FSM - description styles

Three processes (modulo-4 counter)

```
module counter03 ( clk, resetn, three );
    input clk, resetn;
    output three;    reg three;
    reg [1:0] pres_state, next_state;
    always @ (posedge clk) // State memory
        pres_state <= next_state;
    // Next state function
    always @ (resetn or pres_state) begin
        if (resetn==0) next_state = 0;
        else case (pres_state)
            0, 1, 2: next_state = pres_state + 1;
            3:         next_state = 0;
        endcase
    end
    always @ (pres_state) // Output function
        if (pres_state==3) three = 1;
        else               three = 0;
endmodule
```

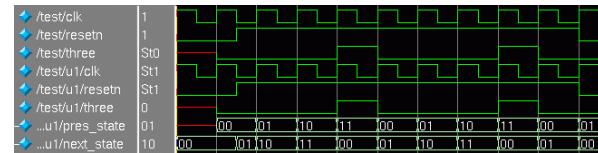


23 gates / 4.36 ns

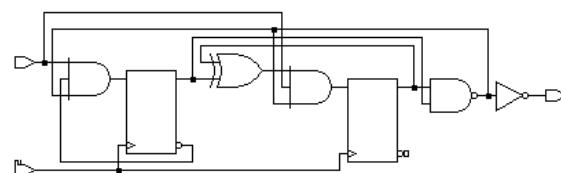


FSM - description styles

Two processes (modulo-4 counter)

```
module counter03 ( clk, resetn, three );
    input clk, resetn;
    output three;    reg three;
    reg [1:0] pres_state, next_state;
    always @ (posedge clk) // State memory
        pres_state = next_state;
    // Next state & output functions
    always @ (resetn or pres_state) begin
        three = 0;
        if (resetn==0) next_state = 0;
        else
            case (pres_state)
                0, 1, 2: next_state = pres_state + 1;
                3: begin next_state = 0; three = 1; end
            endcase
    end
endmodule
```

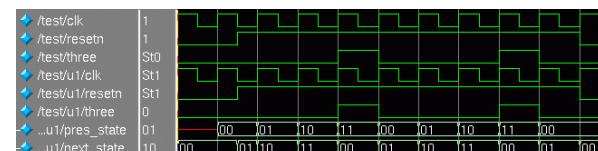

24 gates / 4.36 ns

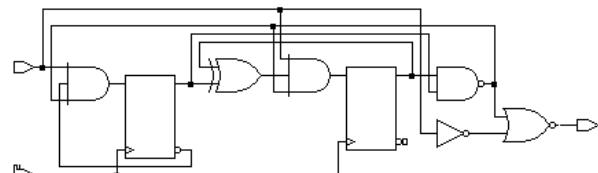




FSM - description styles


One process (modulo-4 counter)

```
module counter03 ( clk, resetn, three );
    input clk, resetn;
    output three;    reg three;
    reg [1:0] state;
    always @(posedge clk) begin
        three = 0;
        if (resetn==0) state = 0;
        else case (state)
            0, 1: state = state + 1;
            2: begin state = state + 1; three = 1; end
            3: state = 0;
        endcase
    end
endmodule

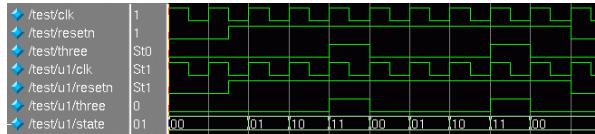// Another version
// to begin the always block
always begin @(posedge clk);
    three = 0; // and so on...
```



38 gates / 5.68 ns

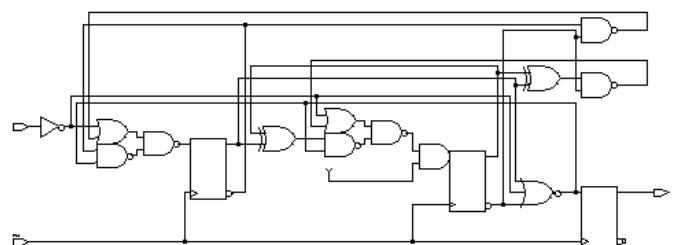


for-loop versus while-loop?

- **Is tool dependent!**
 - Design Compiler (Synopsys) & ISE (Xilinx): **for** - parallel, **while** - parallel
 - No multiple waits!

```
always @ (a or b) begin
    for (i=0;i<4;i=i+1)
        x[i] = a[i] & b[i];
    end
```
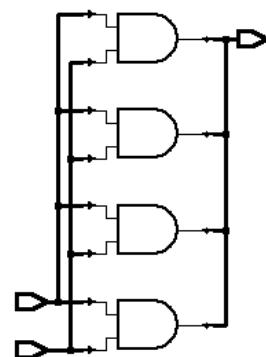
```
always @ (a or b) begin
    i = 0;
    while (i<4) begin
        x[i] = a[i] & b[i];
        i = i + 1;
    end
end
```






Behavioral RTL vs. “pure” RTL

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity test is
    port ( a, b, c: in unsigned(7 downto 0);
           x: in unsigned(2 downto 0);
           o: out unsigned(7 downto 0) );
end test;
architecture bhv of test is begin
process (a, b, c, x)
    constant x2: unsigned(2 downto 0):="010";
    constant x3: unsigned(2 downto 0):="011";
    constant x6: unsigned(2 downto 0):="110";
begin
    if      x=x2 then o <= a+b;
    elsif x=x3 then o <= a+c;
    elsif x=x6 then o <= b+c;
    else          o <= (others=>'0');
    end if;
end process;
end architecture bhv;

module test (a, b, c, x, o);
    input [7:0] a, b, c;
    input [2:0] x;
    output [7:0] o; reg [7:0] o;
    always @(a or b or c or x)
        if      (x==2)  o <= a+b;
        else if (x==3)  o <= a+c;
        else if (x==6)  o <= b+c;
        else          o <= 0;
endmodule // test
```




Behavioral RTL vs. “pure” RTL

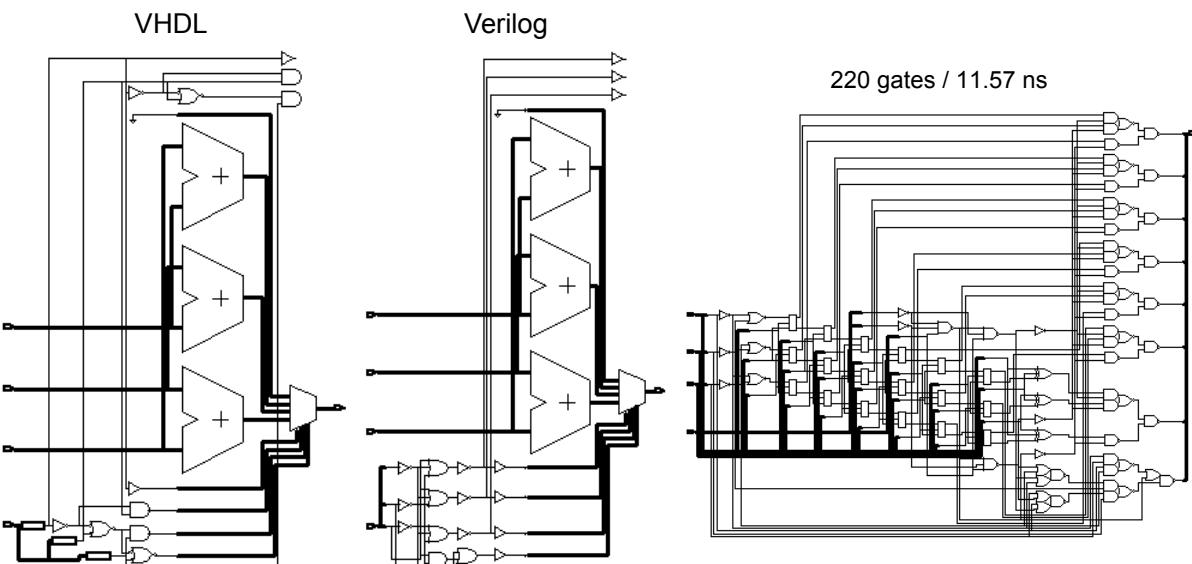


Behavioral RTL vs. “pure” RTL
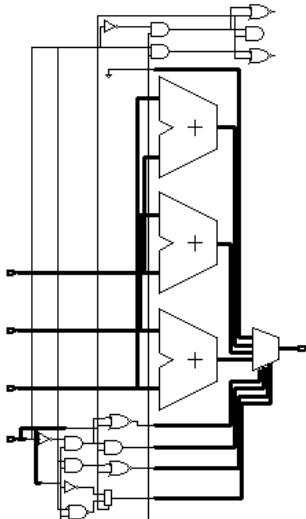
```
architecture bhv2 of test is begin
process (a, b, c, x) begin
    case x is
        when "010" => o <= a+b;
        when "011" => o <= a+c;
        when "110" => o <= b+c;
        when others => o <= (others=>'0');
    end case;
end process;
end architecture bhv2;
```



220 gates / 11.57 ns

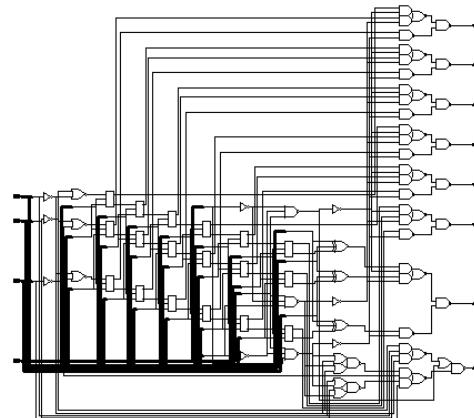


Behavioral RTL vs. “pure” RTL

```
architecture rtl of test is
    signal a1, a2: unsigned(7 downto 0);
    signal dc: unsigned(1 downto 0);
begin
dec: process (x) begin
    case x is
        when "010" => dc <= "01";
        when "011" => dc <= "10";
        when "110" => dc <= "11";
        when others => dc <= "00";
    end case;
end process dec;
m1: process (a, b, dc) begin
    case dc is
        when "01" => a1 <= a;
        when "10" => a1 <= a;
        when "11" => a1 <= b;
        when others => a1 <= (others=>'0');
    end case;
end process m1;
m2: process (b, c, dc) begin
    -- ...
end process m2;
o <= a1 + a2;
end architecture rtl;
```


```
module test (a, b, c, x, o);
    input [7:0] a, b, c;
    input [2:0] x;
    output [7:0] o;
    reg [7:0] a1, a2;
    reg [2:0] dc;
    always @ (x)
        if (x==2) dc = 1;
        else if (x==3) dc = 2;
        else if (x==6) dc = 3;
        else dc = 0;
    always @ (a or b or dc)
        if (dc==1) a1 = a;
        else if (dc==2) a1 = a;
        else if (dc==3) a1 = b;
        else a1 = 0;
    always @ (b or c or dc)
        if (dc==1) a2 = b;
        else if (dc==2) a2 = c;
        else if (dc==3) a2 = c;
        else a2 = 0;
    assign o = a1+a2;
endmodule // test
```




Behavioral RTL vs. “pure” RTL

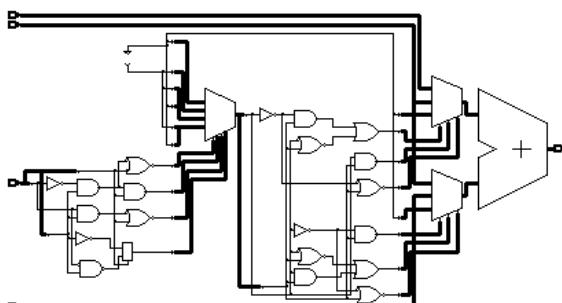

VHDL

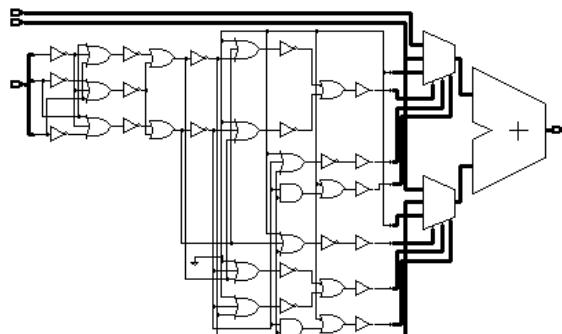

Verilog

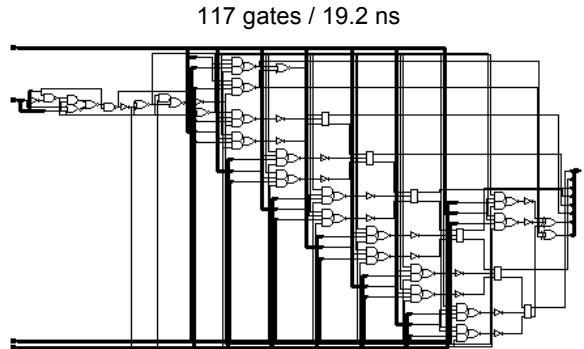

117 gates / 19.2 ns



Adder / Subtractor

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity add_sub is
  port ( a, b: in unsigned(7 downto 0);
         x: in std_logic;
         o: out unsigned(7 downto 0) );
end add_sub;
architecture bhv of add_sub is begin
process (a, b, x) begin
  if x='0' then o <= a+b;
  else          o <= a-b;  end if;
end process;
end architecture bhv;

module add_sub (a, b, x, o);
  input [7:0] a, b;
  input x;
  output [7:0] o;
  assign o = x==0 ? a+b : a-b;
endmodule // add_sub
```

145 gates / 11.64 ns

```
architecture dfl of test5 is
  signal a1, b1, o1: unsigned(8 downto 0);
begin
  a1 <= a & '1';
  b1 <= b & '0' when x='0' else
    unsigned(not std_logic_vector(b)) &
    '1';
  o1 <= a1+b1;
  o <= o1(8 downto 1);
end architecture dfl;
/* ... */
assign {o,t} = {a,1'b1} +
  ( x==0 ? {b,1'b0} : {~b,1'b1} );
```

87 gates / 12.45 ns

