

# **Understanding Verilog Blocking and Non-blocking Assignments**

**International Cadence  
User Group Conference**

**September 11, 1996**

presented by

**Stuart Sutherland**

Sutherland and HDL Consulting

# About the Presenter

Stuart Sutherland has over 8 years of experience using Verilog with a variety of software tools. He holds a BS degree in Computer Science, with an emphasis on Electronic Engineering, and has worked as a design engineer in the defense industry, and as an Applications Engineer for Gateway Design Automation (the originator of Verilog) and Cadence Design Systems. Mr. Sutherland has been providing Verilog HDL consulting services since 1991. As a consultant, he has been actively involved in using the Verilog language with a many different of software tools for the design of ASICs and systems. He is a member of the IEEE 1364 standards committee and has been involved in the specification and testing of Verilog simulation products from several EDA vendors, including the Intergraph-VeriBest *VeriBest* simulator, the Mentor *QuickHDL* simulator, and the Frontline *CycleDrive* cycle based simulator. In addition to Verilog design consulting, Mr. Sutherland provides expert on-site Verilog training on the Verilog HDL language and Programing Language Interface. Mr. Sutherland is the author and publisher of the popular “*Verilog IEEE 1364 Quick Reference Guide*” and the “*Verilog IEEE 1364 PLI Quick Reference Guide*”.

Please conact Mr. Sutherland with any questions about this material!

## Sutherland and HDL Consulting

Verilog Consulting and Training Services

22805 SW 92<sup>nd</sup> Place

Tualatin, OR 97062 USA

phone: (503) 692-0898

fax: (503) 692-1512

e-mail: [stuart@sutherland.com](mailto:stuart@sutherland.com)

## copyright notice

©1996

The material in this presentation is copyrighted by Sutherland HDL Consulting, Tualatin, Oregon. The presentation is printed with permission as part of the proceedings of the 1996 International Cadence User Group Conference. All rights are reserved. No material from this presentation may be duplicated or transmitted by any means or in any form without the express written permission of Sutherland HDL Consulting.

Sutherland HDL Consulting  
22805 SW 92<sup>nd</sup> Place  
Tualatin, OR 97062 USA

phone: (503) 692-0898

fax: (503) 692-1512

e-mail: [info@sutherland.com](mailto:info@sutherland.com)

# Objectives

- The primary objective is to understand:

What type of hardware is represented  
by blocking and non-blocking  
assignments?

- The material presented is a subset of an advanced Verilog HDL training course

# Procedural Assignments

- Procedural assignment evaluation can be modeled as:
  - Blocking
  - Non-blocking
- Procedural assignment execution can be modeled as:
  - Sequential
  - Concurrent
- Procedural assignment timing controls can be modeled as:
  - Delayed evaluations
  - Delayed assignments

# Blocking Procedural Assignments

Sutherland  
HDL

- The `=` token represents a **blocking** procedural assignment
  - Evaluated and assigned in a single step
  - Execution flow within the procedure is blocked until the assignment is completed
  - Evaluations of concurrent statements in the same time step are blocked until the assignment is completed

These examples will *not* work — Why not?

```
//swap bytes in word
always @(posedge clk)
begin
    word[15:8] = word[ 7:0];
    word[ 7:0] = word[15:8];
end
```

```
//swap bytes in word
always @(posedge clk)
fork
    word[15:8] = word[ 7:0];
    word[ 7:0] = word[15:8];
join
```

# Non-Blocking Procedural Assignments

- The `<=` token represents a **non-blocking** assignment
  - Evaluated and assigned in two steps:
    - ① The right-hand side is evaluated immediately
    - ② The assignment to the left-hand side is postponed until other evaluations in the current time step are completed
  - Execution flow within the procedure continues until a timing control is encountered (flow is not blocked)

These examples will work — Why?

```
//swap bytes in word
always @(posedge clk)
begin
    word[15:8] <= word[ 7:0];
    word[ 7:0] <= word[15:8];
end
```

```
//swap bytes in word
always @(posedge clk)
fork
    word[15:8] <= word[ 7:0];
    word[ 7:0] <= word[15:8];
join
```

# Representing Simulation Time as Queues

- Each Verilog simulation time step is divided into 4 queues

## Time 0:

- Q1 — *(in any order)* :
  - Evaluate RHS of all non-blocking assignments
  - Evaluate RHS and change LHS of all blocking assignments
  - Evaluate RHS and change LHS of all continuous assignments
  - Evaluate inputs and change outputs of all primitives
  - Evaluate and print output from \$display and \$write
- Q2 — *(in any order)* :
  - Change LHS of all non-blocking assignments
- Q3 — *(in any order)* :
  - Evaluate and print output from \$monitor and \$strobe
  - Call PLI with reason\_synchronize
- Q4 :
  - Call PLI with reason\_rosynchronize

## Time 1:

...

*Note: this is an abstract view, not how simulation algorithms are implemented*



# Sequential Procedural Assignments

- The order of evaluation is **determinate**
  - A **sequential blocking assignment** evaluates and assigns before continuing on in the procedure

```
always @(posedge clk)
```

```
begin
```

```
    A = 1;
```

← evaluate and assign A immediately

```
    #5 B = A + 1;
```

← delay 5 time units, then evaluate and assign

```
end
```

- A **sequential non-blocking assignment** evaluates, then continues on to the next timing control before assigning

```
always @(posedge clk)
```

```
begin
```

```
    A <= 1;
```

← evaluate A immediately; assign at end of time step

```
    #5 B <= A + 1;
```

← delay 5 time units, then evaluate; then assign at

```
end
```

end of time step (clock + 5)

# Concurrent Procedural Assignments

The order of concurrent evaluation is **indeterminate**

- Concurrent **blocking assignments** have **unpredictable results**

```
always @(posedge clk)
#5 A = A + 1;
```

```
always @(posedge clk)
#5 B = A + 1;
```

**Unpredictable Result:**

(new value of B could be evaluated before or after A changes)

- Concurrent **non-blocking assignments** have **predictable results**

```
always @(posedge clk)
#5 A <= A + 1;
```

```
always @(posedge clk)
#5 B <= A + 1;
```

**Predictable Result:**

(new value of B will always be evaluated before A changes)

# Delayed Evaluation Procedural Assignments

- A timing control before an assignment statement will postpone when the next assignment is evaluated
  - Evaluation is delayed for the amount of time specified

begin

#5 A = 1;

#5 A = A + 1;

B = A + 1;

end

← delay for 5, then evaluate and assign

← delay 5 more, then evaluate and assign

← no delay; evaluate and assign

What values do A and B contain after 10 time units?

# Delayed Assignment

## Procedural Assignments

- An *intra-assignment delay* places the timing control **after** the assignment token
  - The right-hand side is evaluated before the delay
  - The left-hand side is assigned after the delay

always @(A)

B = #5 A;

A is evaluated at the time it changes, but is not assigned to B until after 5 time units

always @(negedge clk)

Q <= @(posedge clk) D;

D is evaluated at the negative edge of CLK, Q is changed on the positive edge of CLK

```
always @(instructor_input)
```

```
  if (morning)
```

```
    understand = instructor_input;
```

```
  else if (afternoon)
```

```
    understand = #5 instructor_input;
```

```
  else if (lunch_time)
```

```
    understand = wait (!lunch_time) instructor_input;
```

# Intra-Assignment Delays With Repeat Loops

- An edge-sensitive intra-assignment timing control permits a special use of the repeat loop
  - The edge sensitive time control may be repeated several times before the delay is completed
  - Either the blocking or the non-blocking assignment may be used

```
always @(IN)  
  OUT <= repeat (8) @(posedge clk) IN;
```

The value of **IN** is evaluated when it changes, but is not assigned to **OUT** until after 8 clock cycles

# Choosing the Correct Procedural Assignment

- Which procedural assignment should be used to model a combinatorial logic buffer?

```
always @(in)
  #5 out = in;
```

```
always @(in)
  #5 out <= in;
```

```
always @(in)
  out = #5 in;
```

```
always @(in)
  out <= #5 in;
```

- Which procedural assignment should be used to model a sequential logic flip-flop?

```
always @(posedge clk)
  #5 q = d;
```

```
always @(posedge clk)
  #5 q <= d;
```


```
always @(posedge clk)
  q = #5 d;
```

```
always @(posedge clk)
  q <= #5 d;
```


- The following pages will answer these questions
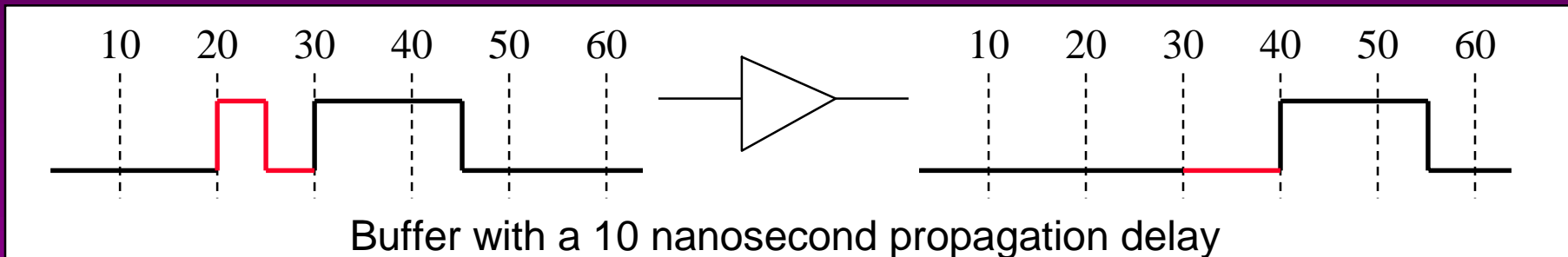
# Transition Propagation Methods

- Hardware has two primary propagation delay methods:
  - **Inertial delay** models devices with finite switching speeds; input glitches do not propagate to the output




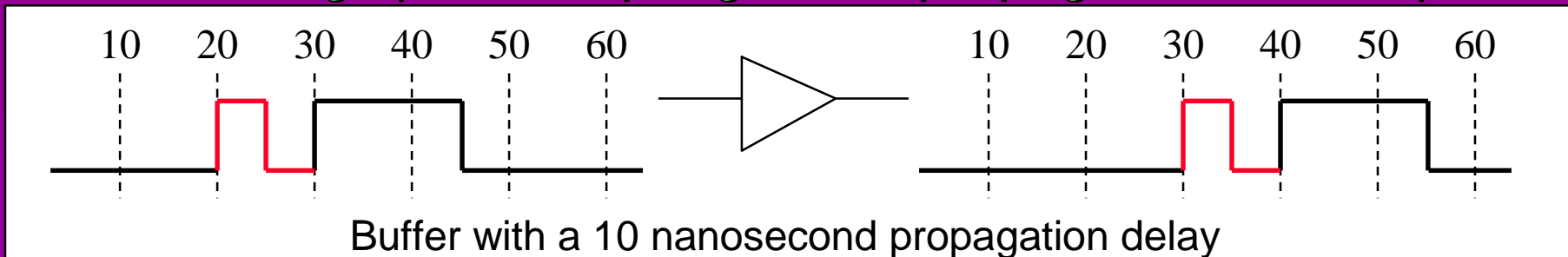- **Transport delay** models devices with near infinite switching speeds; input glitches propagate to the output




# Combinational Logic Procedural Assignments
 
## ► How will these procedural assignments behave?



Blocking, No delay	always @(in) o1 = in;
Non-blocking, No delay	always @(in) o2 <= in;
Blocking, Delayed evaluation	always @(in) #5 o3 = in;
Non-blocking, Delayed evaluation	always @(in) #5 o4 <= in;
Blocking, Delayed assignment	always @(in) o5 = #5 in;
Non-blocking, Delayed assignment	always @(in) o6 <= #5 in;

 




 
# Sequential Logic Procedural Assignments

- How will these procedural assignments behave?
  - Sequential assignments
  - No delays


```
always @(posedge clk)
begin
  y1 = in;
  y2 = y1;
end
```




parallel flip-flops

 
 
```
always @(posedge clk)
begin
  y1 <= in;
  y2 <= y1;
end
```



shift-register with zero delays

 


# Sequential Logic Procedural Assignments

Sutherland  
HDL

 
## ➤ How will these procedural assignments behave?

- Sequential assignments
- Delayed evaluation


```
always @(posedge clk)
begin
    #5 y1 = in;
    #5 y2 = y1;
end
```




shift register with delayed clocks

 
 
```
always @(posedge clk)
begin
    #5 y1 <= in;
    #5 y2 <= y1;
end
```



shift register with delayed clocks

 


# Sequential Logic Procedural Assignments
 
## ➤ How will these procedural assignments behave?


- Sequential assignments
- Delayed assignment

```
always @(posedge clk)
begin
  y1 = #5 in;
  y2 = #5 y1;
end
```




shift register delayed clock on second stage
 
```
always @(posedge clk)
begin
  y1 <= #5 in;
  y2 <= #5 y1;
end
```



shift register with delays

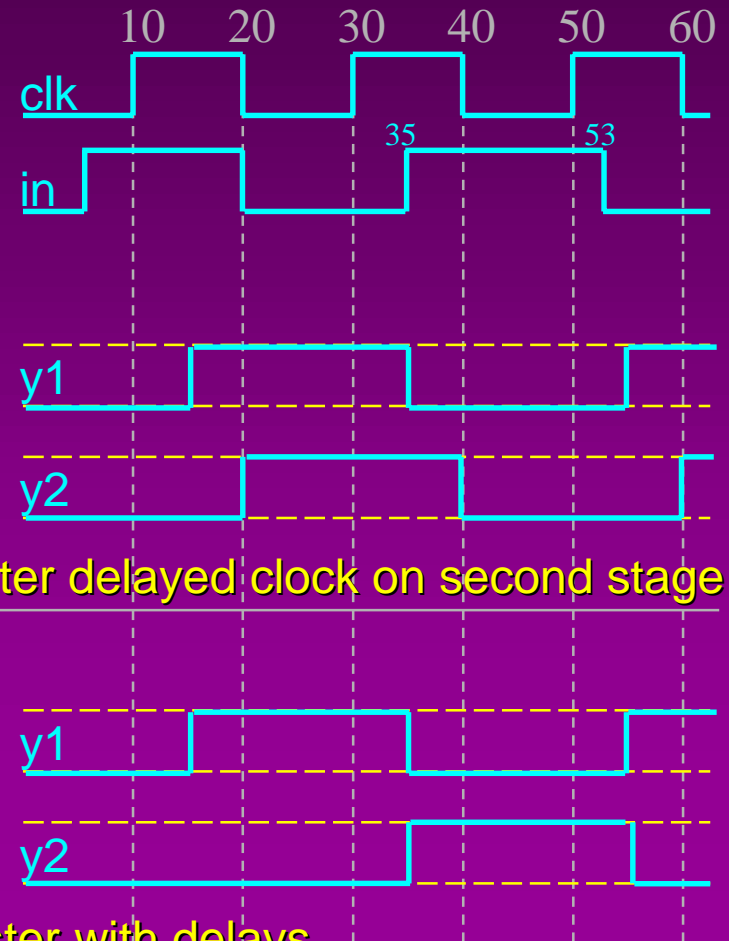

# Sequential Logic

## Procedural Assignments

Sutherland and  
HDL



### ➤ How will these procedural assignments behave?

#### ➤ Concurrent assignments

#### ➤ No delays

```
always @(posedge clk)
  y1 = in;
```



```
always @(posedge clk)
  y2 = y1;
```

  

shift register with race condition

```
always @(posedge clk)
  y1 <= in;
```
  
```
always @(posedge clk)
  y2 <= y1;
```



shift-register with zero delays



# Sequential Logic Procedural Assignments

## ➤ How will these procedural assignments behave?

- Concurrent assignments
- Delayed evaluation

```
always @(posedge clk)
  #5 y1 = in;
```

 
 
```
always @(posedge clk)
  #5 y2 = y1;
```



shift register with race condition

```
always @(posedge clk)
  #5 y1 <= in;
```
  
```
always @(posedge clk)
  #5 y2 <= y1;
```



shift register with race condition

# Sequential Logic

## Procedural Assignments


Sutherland  
HDL

### ➤ How will these procedural assignments behave?

- Concurrent assignments
- Delayed assignment

```
always @(posedge clk)
  y1 = #5 in;
```

 
```
always @(posedge clk)
  y2 = #5 y1;
```




shift register, delay must be < clock period

```
always @(posedge clk)
  y1 <= #5 in;
```
 
```
always @(posedge clk)
  y2 <= #5 y1;
```



shift register with delays

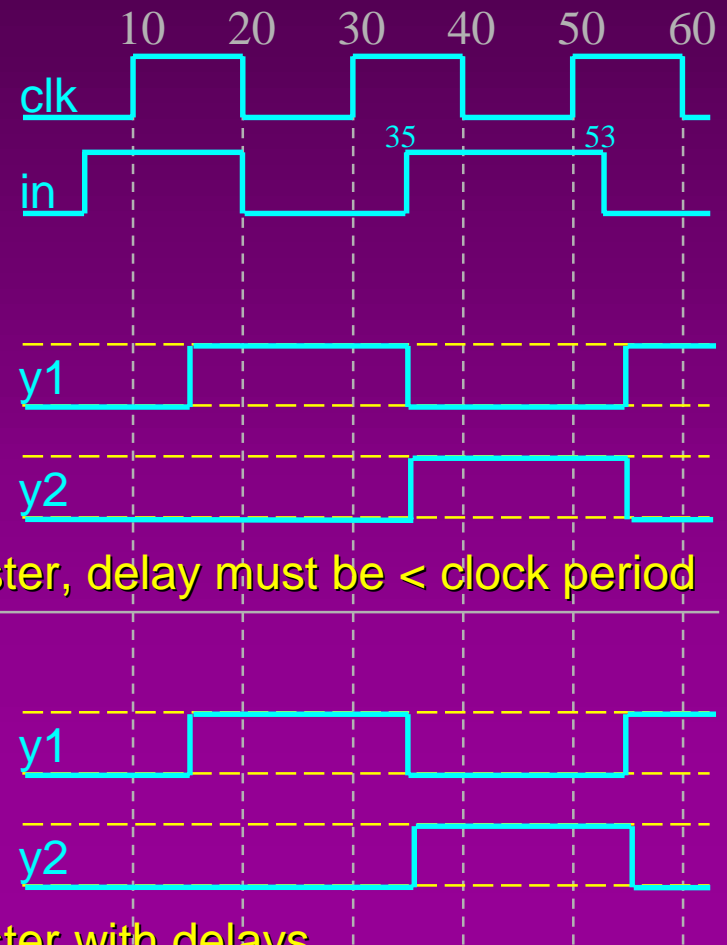

# Rules of Thumb for Procedural Assignments

## ➤ Combinational Logic:

- **No delays:** Use blocking assignments ( `a = b;` )
- **Inertial delays:** Use delayed evaluation blocking assignments ( `#5 a = b;` )
- **Transport delays:** Use delayed assignment non-blocking assignments ( `a <= #5 b;` )

## ➤ Sequential Logic:

- **No delays:** Use non-blocking assignments ( `q <= d;` )
- **With delays:** Use delayed assignment non-blocking assignments ( `q <= #5 d;` )

# An Exception to Non-blocking Assignments in Sequential Logic

- Do **not** use a non-blocking assignment if another statement in the procedure requires the new value in the same time step

```
begin
  #5 A <= 1;
  #5 A <= A + 1;
  B <= A + 1;
end
```

What values do **A** and **B** contain after 10 time units? **A is 2 B is 2**

```
always @(posedge clk)
begin
  case (state)
    `STOP: next_state <= `GO;
    `GO: next_state <= `STOP;
  endcase
  state <= next_state;
end
```

Assume **state** and **next\_state** are **`STOP** at the first clock, what is **state**:

- At the 2nd clock? **`STOP**
- At the 3rd clock? **`GO**
- At the 4th clock? **`GO**
- At the 5th clock? **`STOP**



## Exercise 3: Procedural Assignments

- Write a procedure for an adder (combinational logic) that assigns C the sum of A plus B with a 7ns propagation delay.

```
always @(A or B)
  #7 C = A + B;
```

- Write the procedure(s) for a 4-bit wide shift register (positive edge triggered) of clock and has a 4ns propagation delay.

```
always @(posedge clk)
begin
  y1 <= #4 in;
  y2 <= #4 y1;
  y3 <= #4 y2;
  out <= #4 y3;
end
```


```
always @(posedge clk)
  y1 <= #4 in;
always @(posedge clk)
  y2 <= #4 y1;
always @(posedge clk)
  y3 <= #4 y2;
always @(posedge clk)
  out <= #4 y3;
```
 
## Exercise 3 (continued): Procedural Assignments

- Write a Verilog procedure for a “black box” ALU pipeline that takes 8 clock cycles to execute an instruction. The pipeline triggers on the positive edge of clock. The “black box” is represented as call to a function named ALU with inputs A, B and OPCODE.



How many Verilog statements does it take to model an eight stage pipeline?



```
always @(posedge clk)
  alu_out <= repeat(7) @(posedge clk) ALU(A,B,OPCODE);
```